

Battery Monitor Project


12V Battery Monitor For Simple Battery Status

WØLIC & KCØRPS
285 TechConnect Club
June 7, 2014



Credits


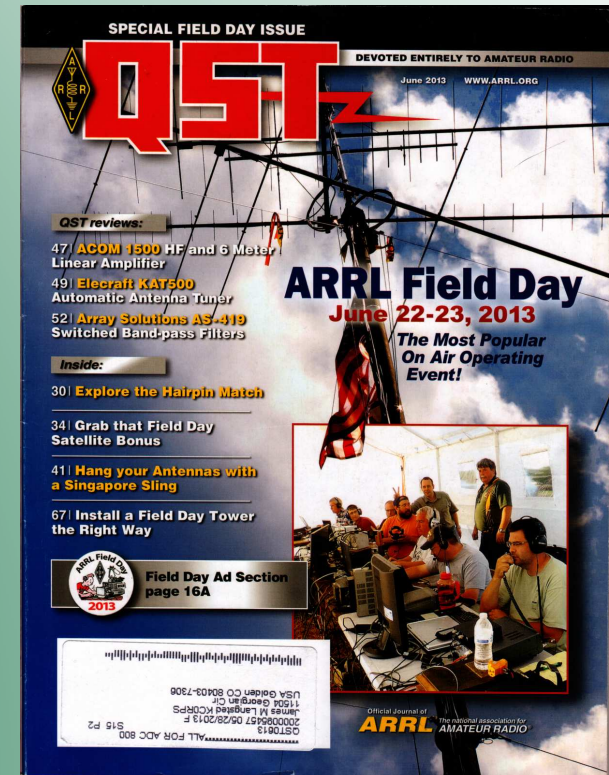
- Mert Nellis W0UFO
- QST June 2013, p.43
- Callard & Bowser, Chicago IL



Overview


- Application
 - Monitor battery status under load
 - Monitor battery charge status with solar panel
- Features
 - Green, Orange, Yellow, Red indicator
 - Pocket size

Construction Methods

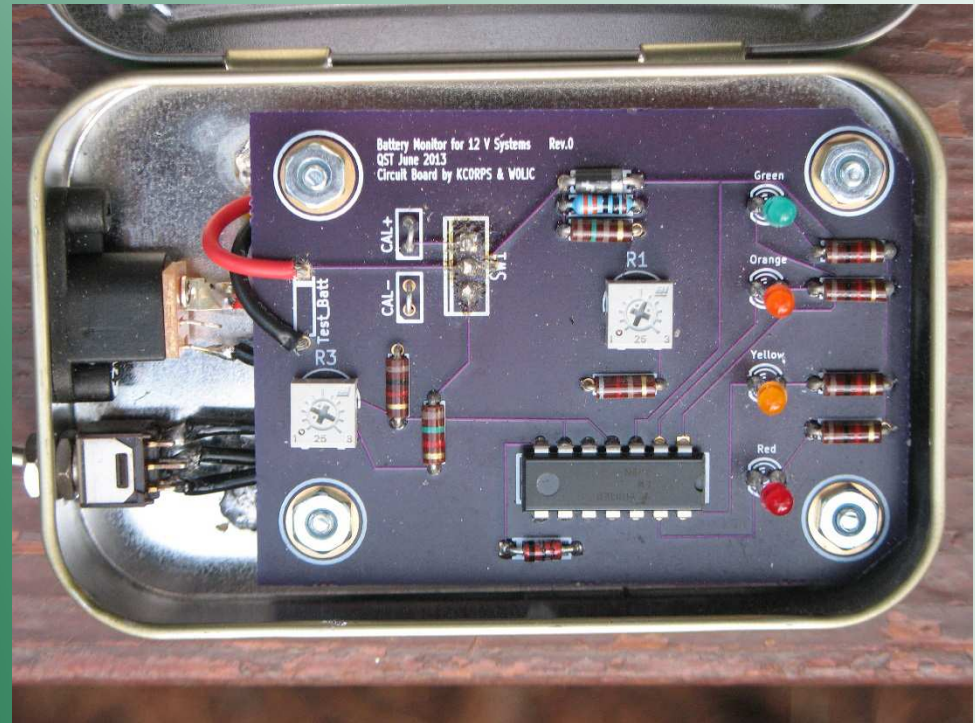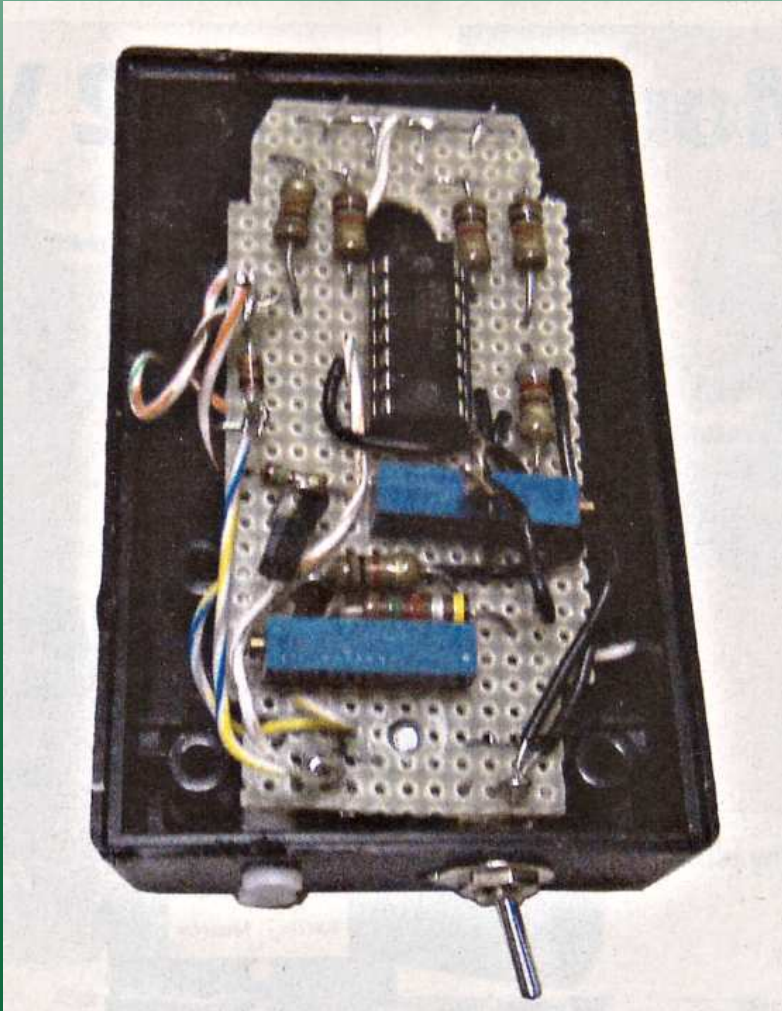


Operation

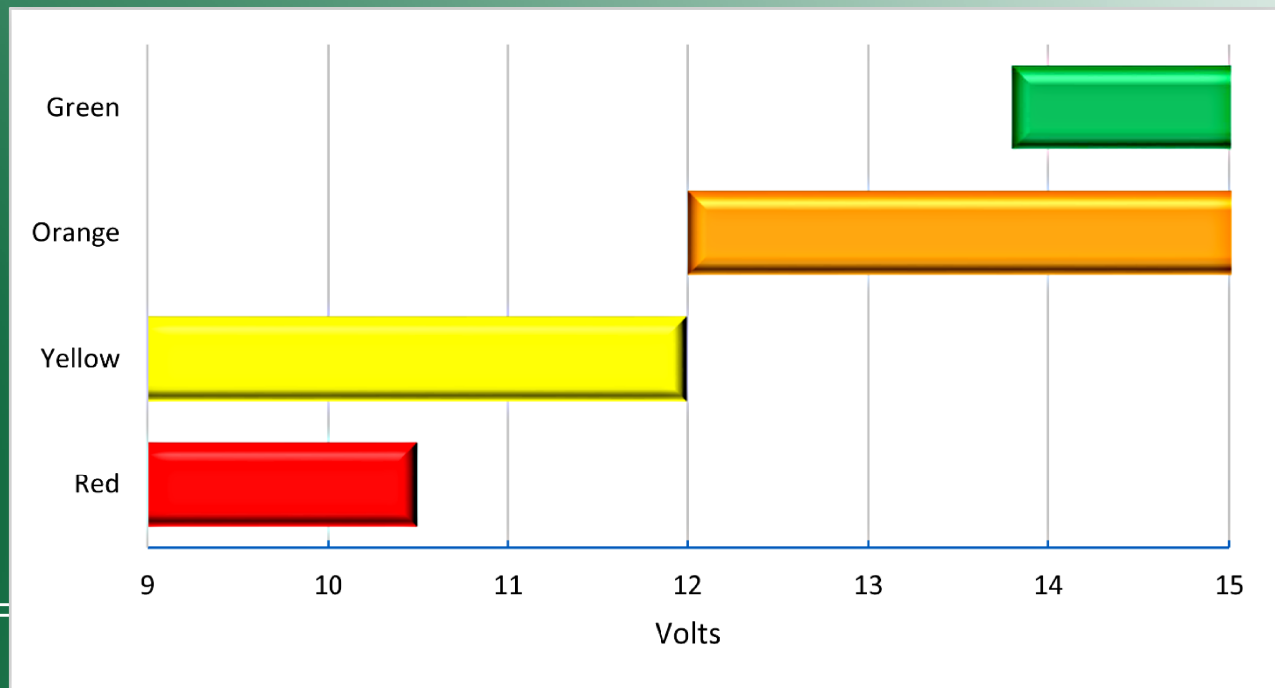- Orange + Green = 13.8V (adjustable)
- Orange >12V
- Yellow <12V
- Yellow + Red = 10.5V (adjustable)



Circuit Analysis

5V Ref. Resistor String

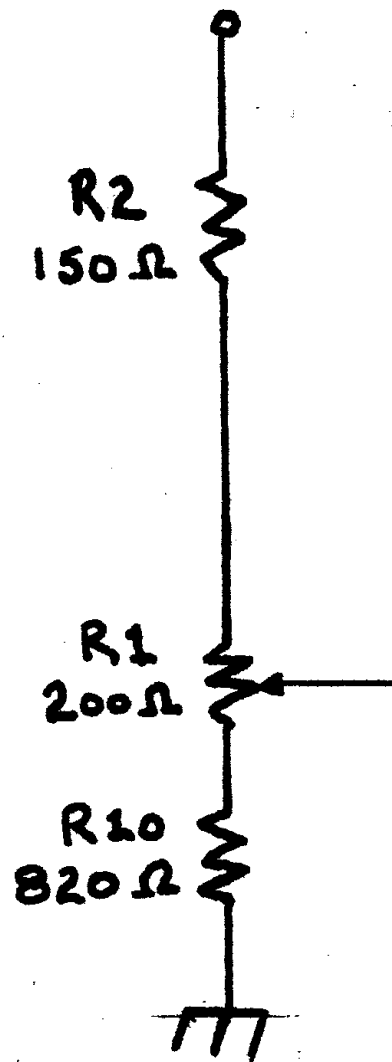

To find the voltage at any point on a resistor string, divide the resistance to ground at the point of interest by the total resistance of the string times the string voltage.

Example: Find the wiper voltage when measured at the mid-point of R_1 .

$$V(w) = (820 + 100) / 1170 \times 5 = 3.93V$$

Construction

- PC Board
 - KiCad designed
 - Advanced Circuits - \$397 for 5 boards (3-day)
 - OSH Park - \$27.50 for 3 boards (2x2-3/4 inch)
 - Iteed Studios – \$9.90 for 10 boards (5x5 cm)
- Mounting board
 - Drill through
 - Solder to tin
- Drilling Holes (connector & switch)
 - template

Cost

- Mouser Parts - \$12.00
- PC Board - \$0.99
- Metal Enclosure - \$2.49
 - Includes Curiously Strong Mints

The End