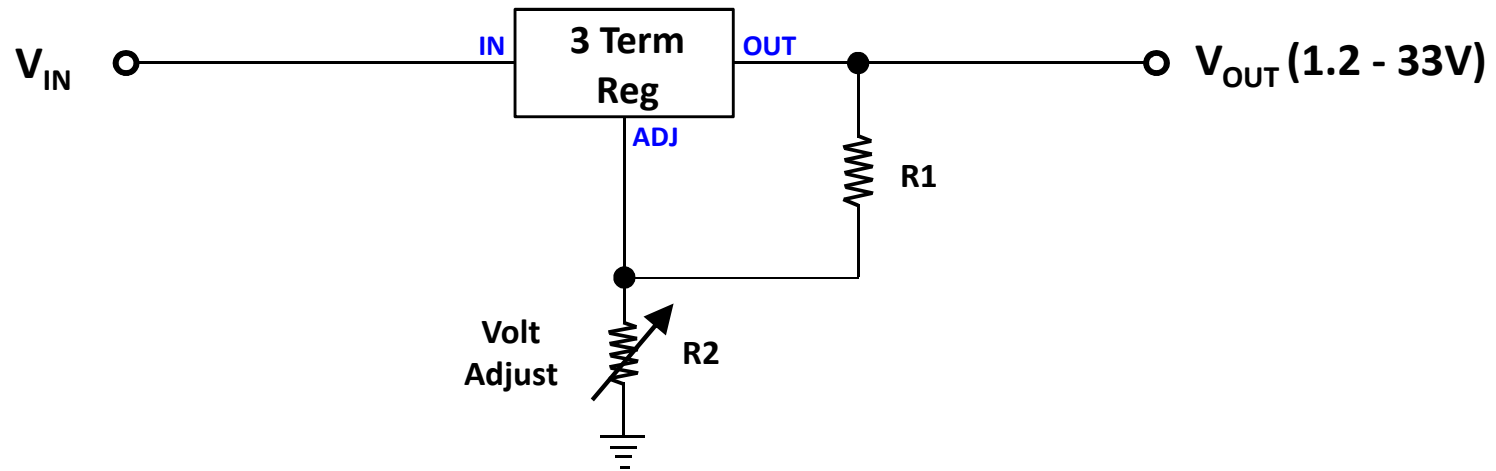


Three Terminal Regulators & Overvoltage Protection


Bill Leonard NOCU

Three Terminal Regulators 101



- Current & power dissipation limits vary with P/N & case style
- Available for both positive and negative supplies
- Maximum current is internally limited
- Case temperature is internally limited
- $V_{OUT} = V_{REF} \times (1 + R2/R1) \approx 1.25 \times (1 + R2/R1)$
 - $R2 \approx R1 \times (V_{OUT} - 1.25) / 1.25$
 - Recommended $R1 = 240 \Omega$
 - $R2 \approx 192 \times (V_{OUT} - 1.25)$
- MANY uses besides voltage regulation (see data sheet)

Three Terminal Regulators - Gotchas

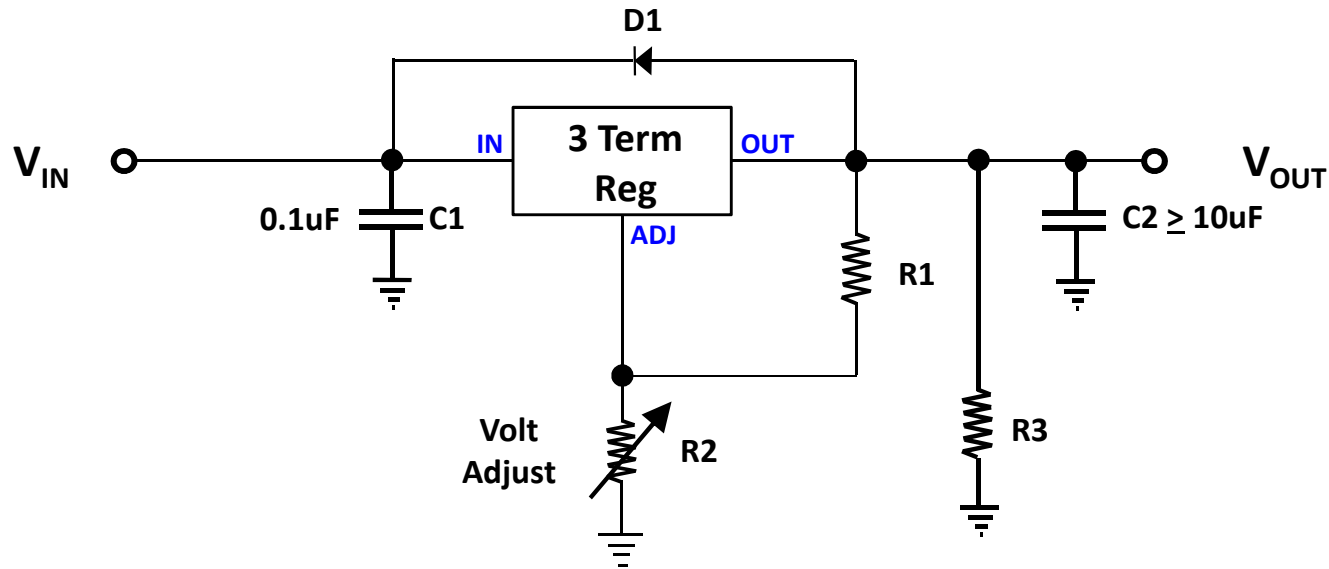


- $C1$ is needed to insure stability (ie, no oscillations)
- $C2$ improves transient response
- $D1$ is needed to protect regulator
- $V_{IN} - V_{OUT} > 2.5 \text{ V}$ (Spec)
- Case is usually connected to V_{OUT}
- $R3$ may/may not be required
 - I_{OUT} must always be $> 10 \text{ mA}$ (Spec) for regulation to occur

Why Add Overvoltage Protection (OVP)?

- Whenever the cost of the load exceeds the cost of OVP
- Transients on AC power line
- Warranty concerns with new transceivers
 - Commercial Power Supplies May Not Have Adequate Protection
 - From eHam reviews: **MFJ-4245MV Switching Power Supply**:
 - “MFJ-4245 is falsely advertising that this power supply has an overvoltage protection per specs....output went to about 35 volts! My IC-735 is now fried.”
 - “...my NEW FT950 transceiver was damaged.”
 - “...it burned up my 2m Rig...”
 - “**If you touch the output leads together**, your 13 volt supply suddenly puts out 33 volts.”

Typical Overvoltage Protection Approach

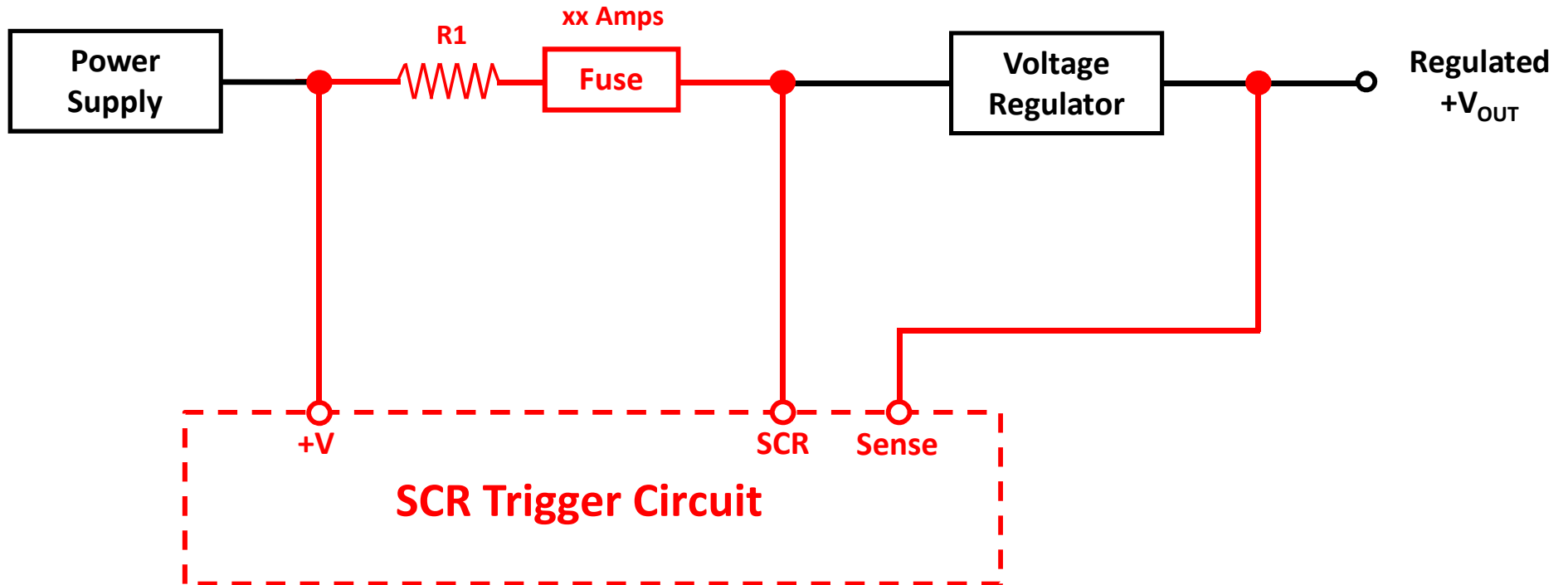

Response Time of Fuses

- Fuses open based upon “**energy**” dissipated in the fuse
 - Ampere squared seconds (I^2t):

“The melting, arcing, or clearing integral of a fuse, termed I^2t , is the thermal energy required to melt, arc, or clear a specific current. It can be expressed as melting I^2t , arcing I^2t or the sum of them, clearing I^2t .”
- UL listed or recognized fast acting fuses would typically open within **5 seconds** maximum when subjected to **200% to 250% of its rated current**.

Overvoltage Protection Circuit in ARRL Handbook

From ARRL Handbook 2004 page 11.39

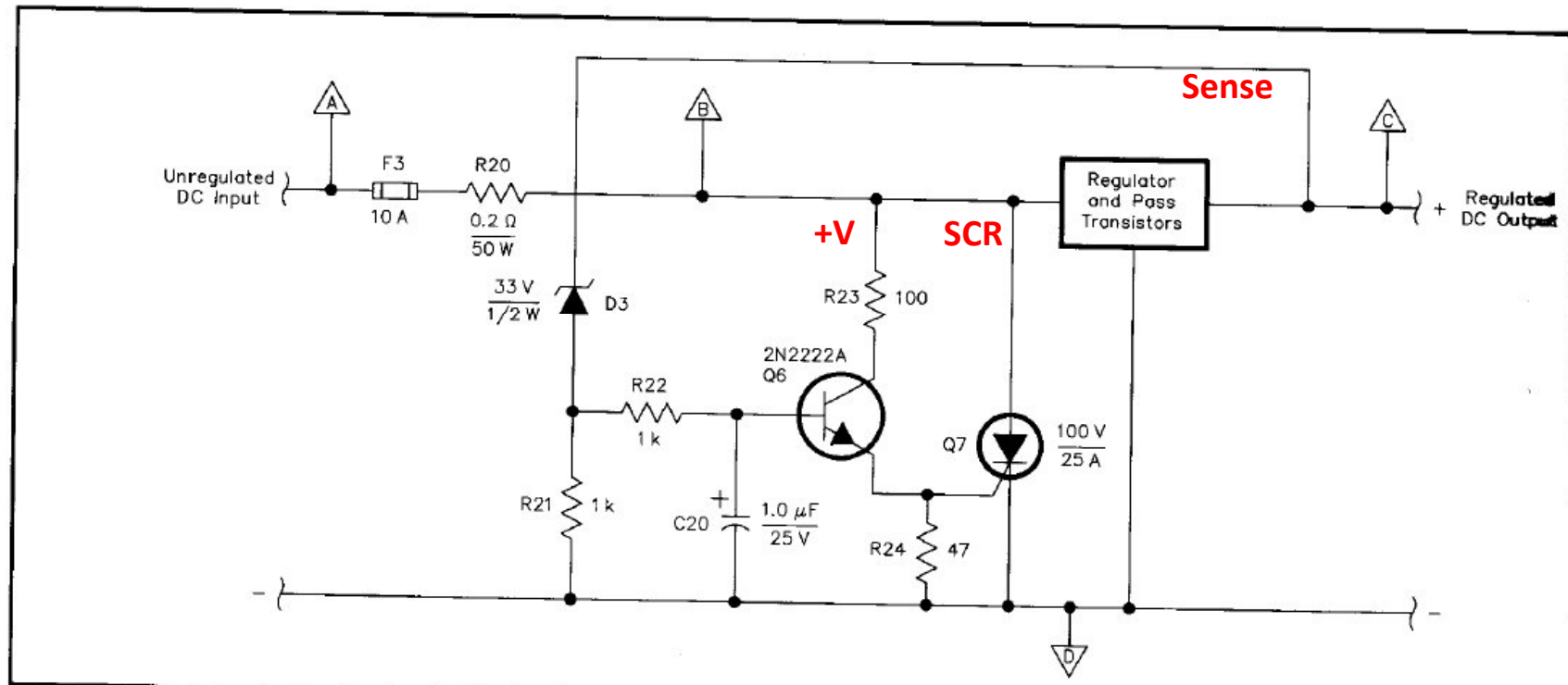


Fig 11.51 — Schematic diagram of the overvoltage protection circuit. Resistors are 1/4-W, 5% carbon types unless noted.
D3 — 33 V, 1/2 W Zener (NTE 5036A or equiv.).
Q6 — NPN Transistor (2N2222A or equiv.).
Q7 — 100 V, 25A SCR (NTE 5522 or equiv.).

Overvoltage Protection Circuit in ARRL Handbook

From ARRL Handbook 2004 page 11.39


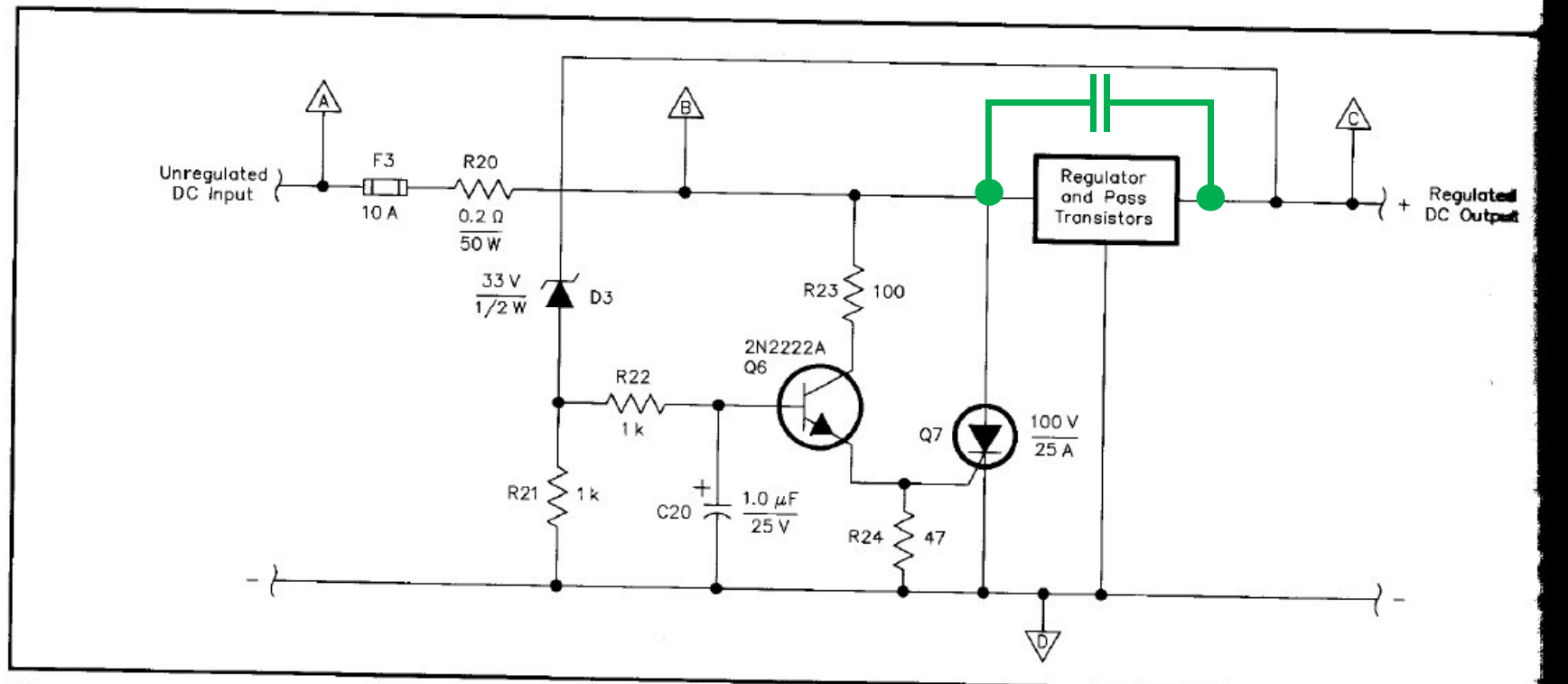
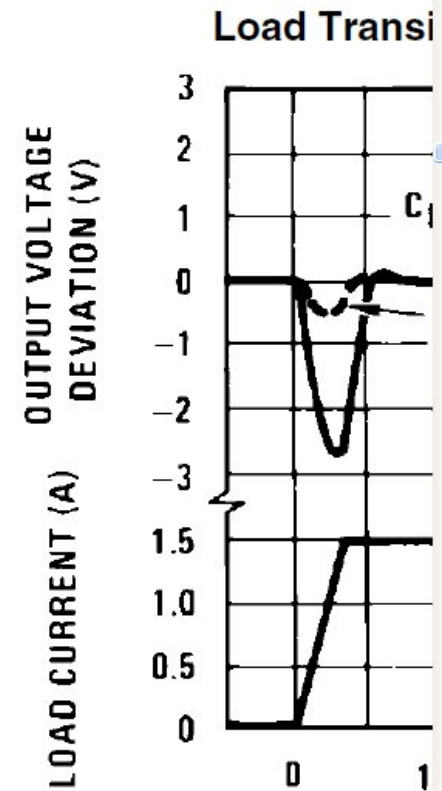


Fig 11.51 — Schematic diagram of the overvoltage protection circuit. Resistors are 1/4-W, 5% carbon types unless noted.
D3 — 33 V, 1/2 W Zener (NTE 5036A or equiv.).
Q6 — NPN Transistor (2N2222A or equiv.).
Q7 — 100 V, 25A SCR (NTE 5522 or equiv.).

Problem 1: Transient Feedthru in Voltage Regulators


Transient Feedthru in Voltage Regulators

LM117/LM317A/LM317

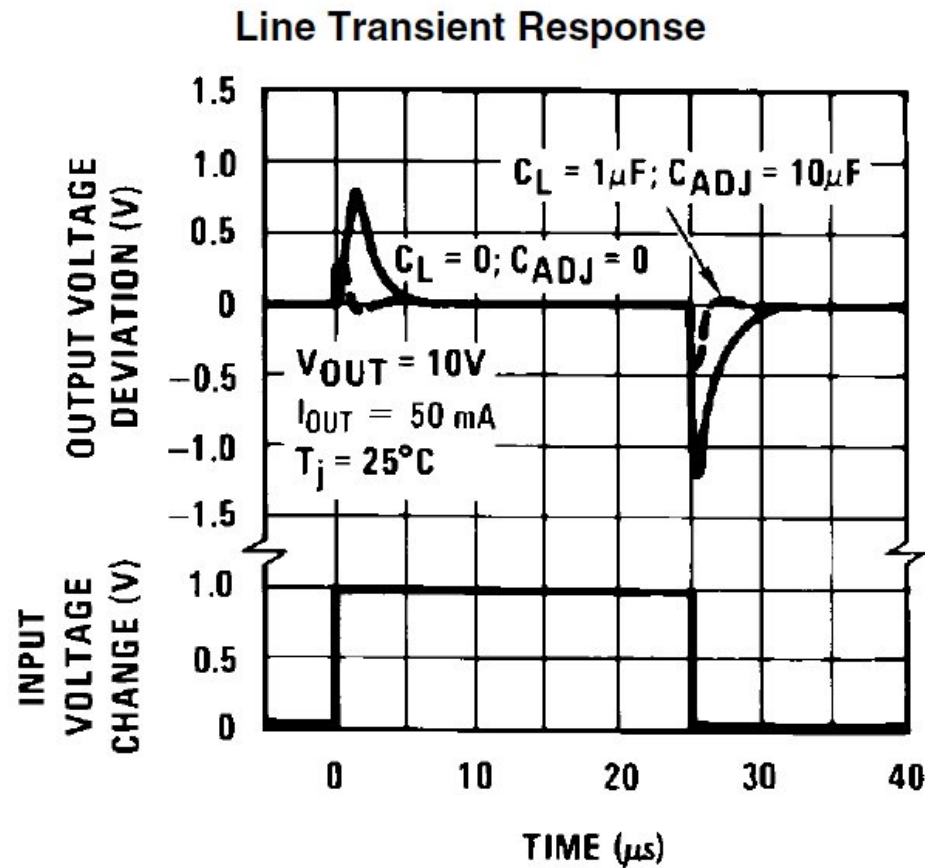

To Reduce Transient Feedthru in Voltage Regulators

Make $(R1 \times C1) > 100 \text{ usec}$

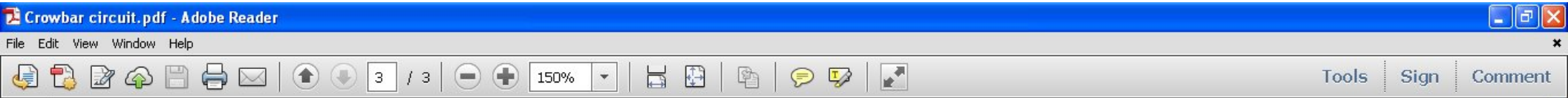

From ARRL Handbook 2004 page 11.39


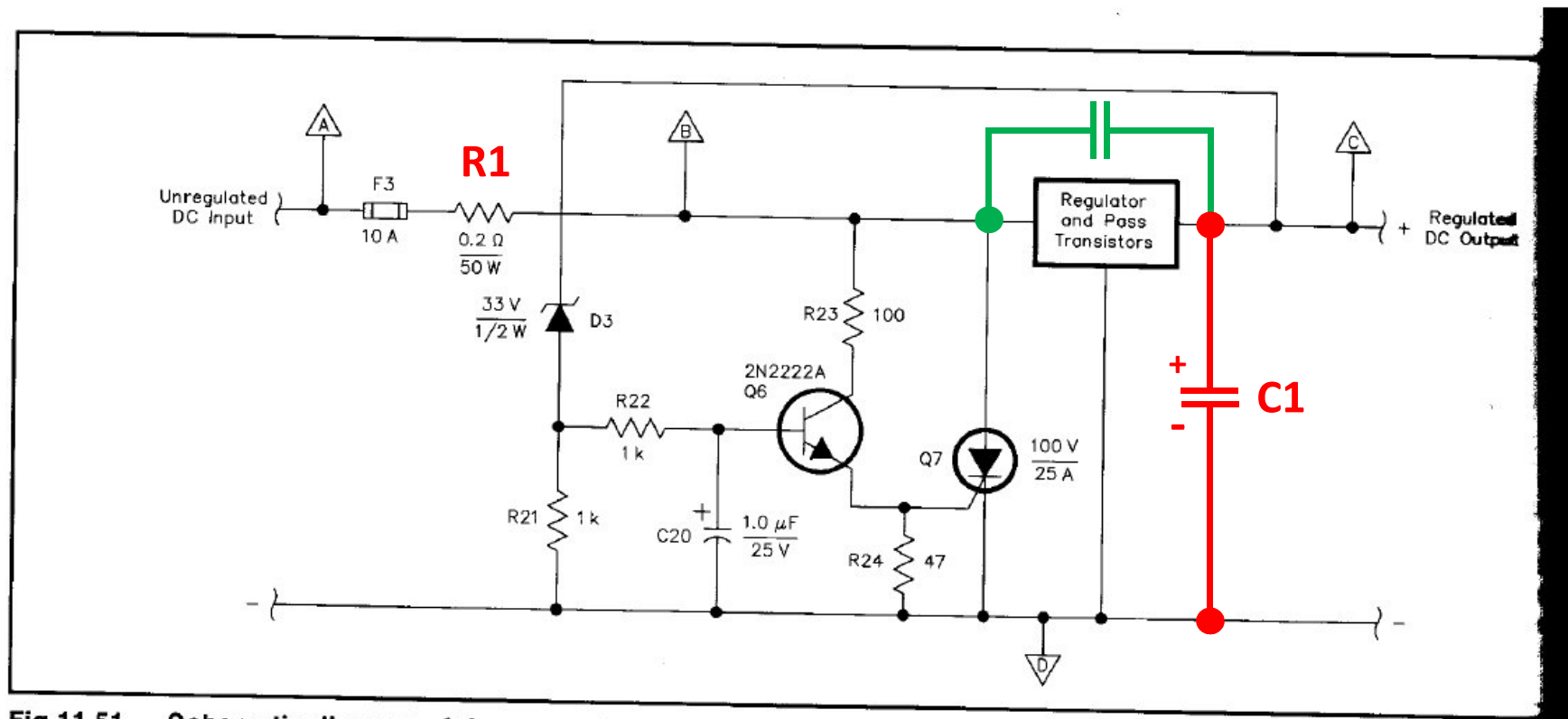


Fig 11.51 — Schematic diagram of the overvoltage protection circuit. Resistors are 1/4-W, 5% carbon types unless noted.
D3 — 33 V, 1/2 W Zener (NTE 5036A or equiv.).
Q6 — NPN Transistor (2N2222A or equiv.).
Q7 — 100 V, 25A SCR (NTE 5522 or equiv.).


Overvoltage Protection Circuit in ARRL Handbook

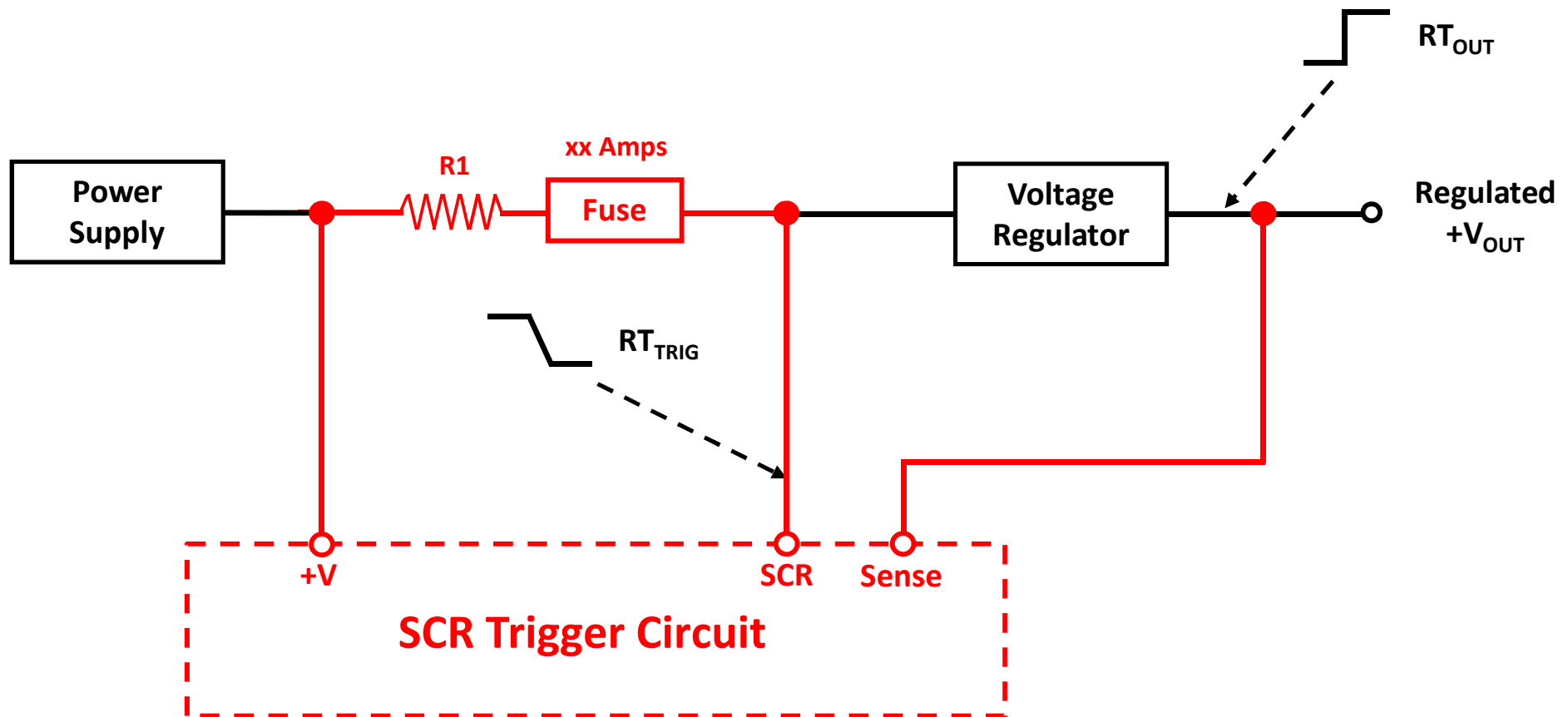

Problem 2: Two critical response times need to be addressed or the protection circuit *may not protect the load*

- Response Time at $+V_{OUT}$ (RT_{OUT})
- Response Time of the Trigger Circuit (RT_{TRIG})


Response Time At Output (RT_{OUT})

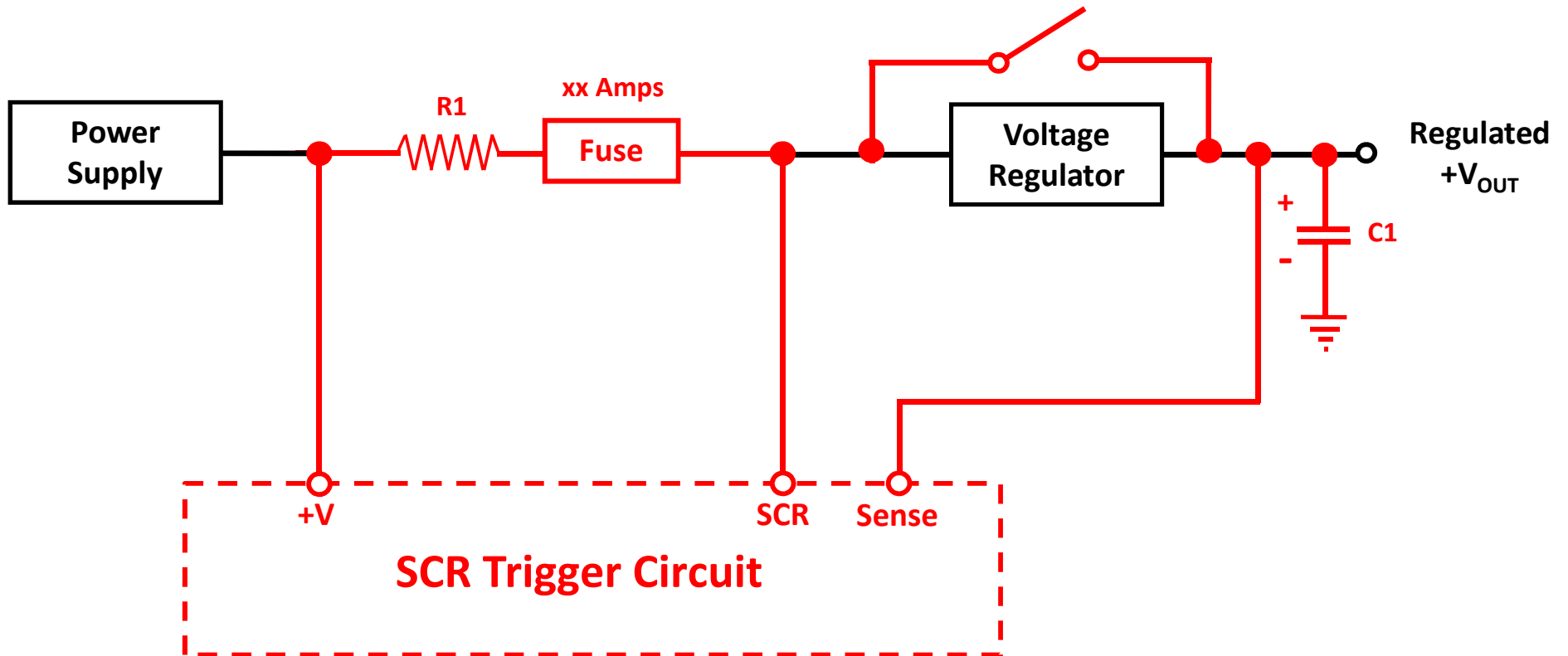

- $RT_{OUT} \approx RT1 \approx R1 \times C1$
 - No $C1$ specified $\Rightarrow RT1 = R1 \times C1 = R1 \times 0 = 0$

Response Time of the Trigger Circuit (RT_{TRIG})

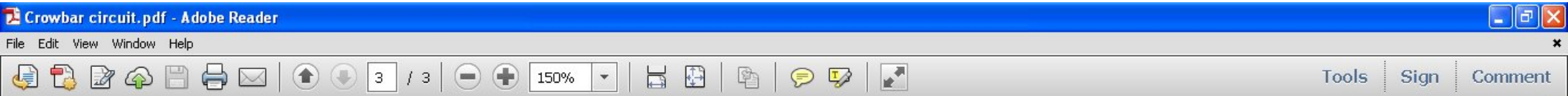- $RT_{TRIG} = RT_{SCR} + RT_2 \approx RT_{SCR} + R_2 \times C_2 \approx 1 \text{ usec} + R_2 \times C_2$



From ARRL Handbook 2004 page 11.39

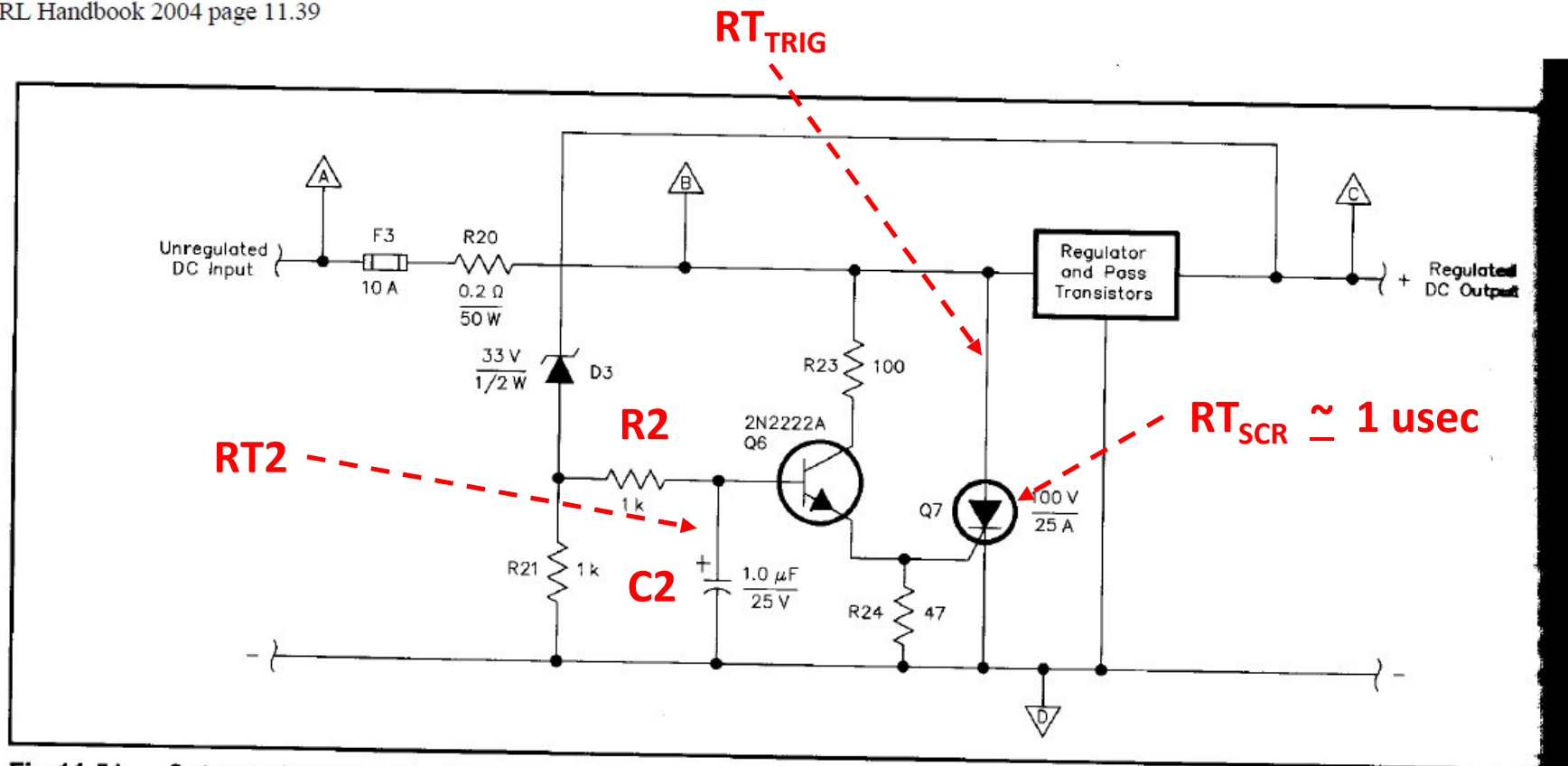


Fig 11.51 — Schematic diagram of the overvoltage protection circuit. Resistors are 1/4-W, 5% carbon types unless noted.
D3 — 33 V, 1/2 W Zener (NTE 5036A or equiv.).
Q6 — NPN Transistor (2N2222A or equiv.).
Q7 — 100 V, 25A SCR (NTE 5522 or equiv.).

Response Time of the Trigger Circuit (RT_{TRIG})

$$RT_2 \approx R_2 \times C_2 = 1000 \text{ ohms} \times 0.000001 \text{ Farad} = 0.001 \text{ sec} = 1 \text{ msec}$$

Crowbar circuit.pdf - Adobe Reader

File Edit View Window Help



Tools Sign Comment

From ARRL Handbook 2004 page 11.39


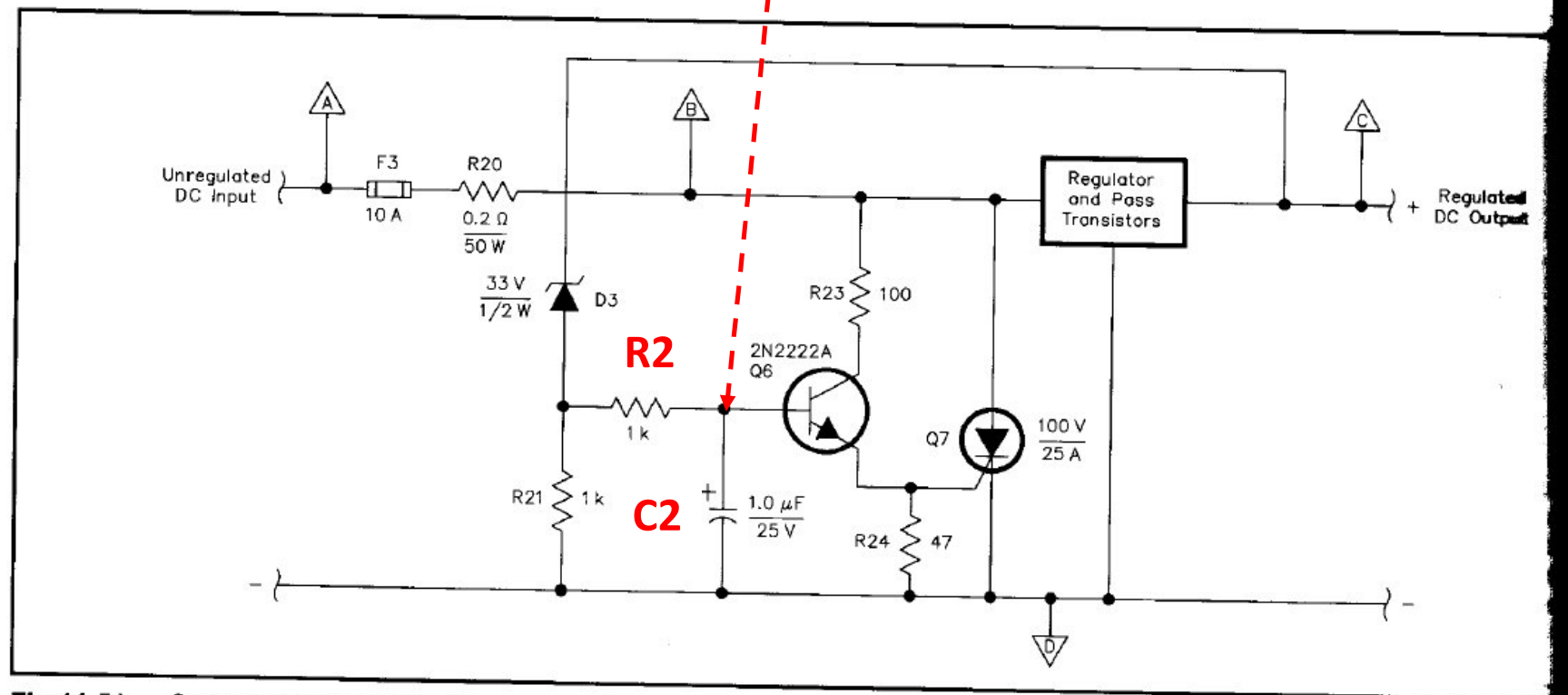


Fig 11.51 — Schematic diagram of the overvoltage protection circuit. Resistors are 1/4-W, 5% carbon types unless noted.
D3 — 33 V, 1/2 W Zener (NTE 5036A or equiv.).
Q6 — NPN Transistor (2N2222A or equiv.).
Q7 — 100 V, 25A SCR (NTE 5522 or equiv.).

Response Time of the Trigger Circuit (RT_{TRIG})
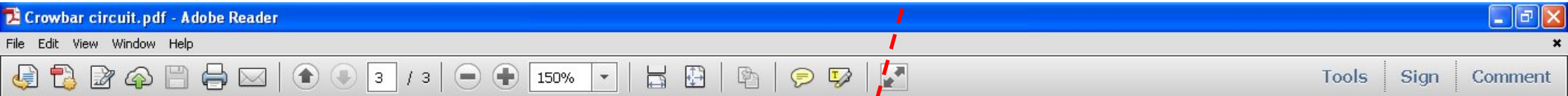
$$RT_2 \approx R_2 \times C_2 = 1 \text{ usec}$$



From ARRL Handbook 2004 page 11.39

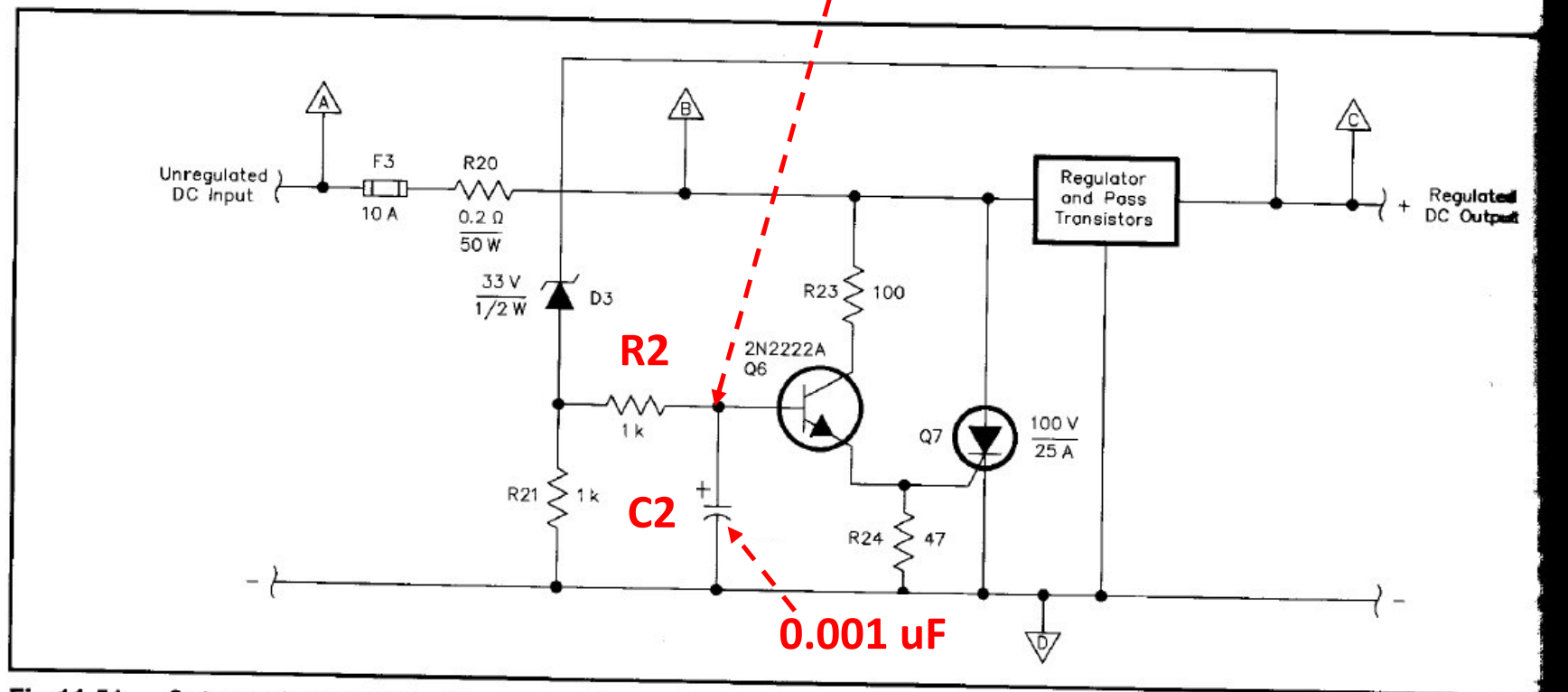


Fig 11.51 — Schematic diagram of the overvoltage protection circuit. Resistors are 1/4-W, 5% carbon types unless noted.
D3 — 33 V, 1/2 W Zener (NTE 5036A or equiv.).
Q6 — NPN Transistor (2N2222A or equiv.).
Q7 — 100 V, 25A SCR (NTE 5522 or equiv.).

Design Goal for Response Times

- $RT1 > 10 \times RT_{TRIG}$

$$RT2 \approx 1 \text{ usec}$$

$$RT1 \approx R1 \times C1$$

Crowbar circuit.pdf - Adobe Reader

File Edit View Window Help



Tools Sign Comment

From ARRL Handbook 2004 page 11.39


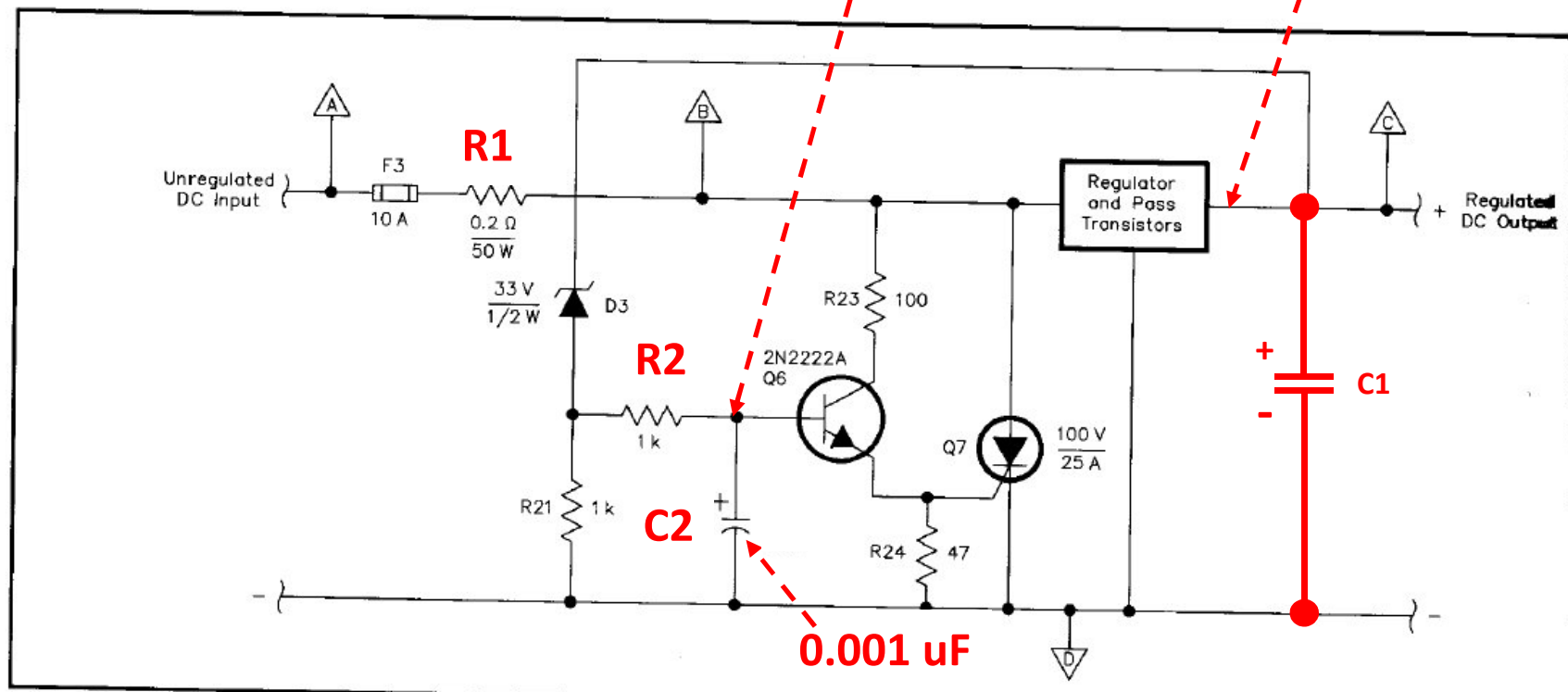



Fig 11.51 — Schematic diagram of the overvoltage protection circuit. Resistors are 1/4-W, 5% carbon types unless noted.
D3 — 33 V, 1/2 W Zener (NTE 5036A or equiv.).
Q6 — NPN Transistor (2N2222A or equiv.).
Q7 — 100 V, 25A SCR (NTE 5522 or equiv.).

Overvoltage Protection Circuit in ARRL Handbook

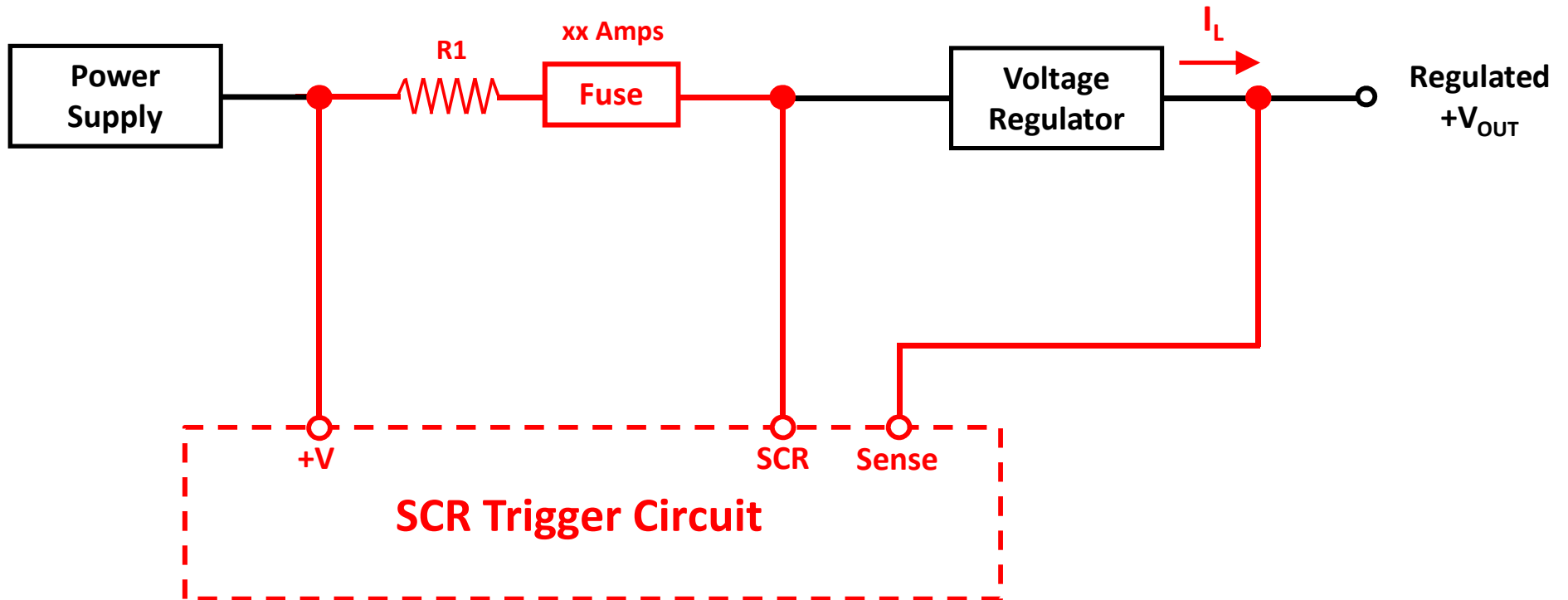


Problem 3: No specified minimum load current (I_L)

Overvoltage Protection Circuit in ARRL Handbook

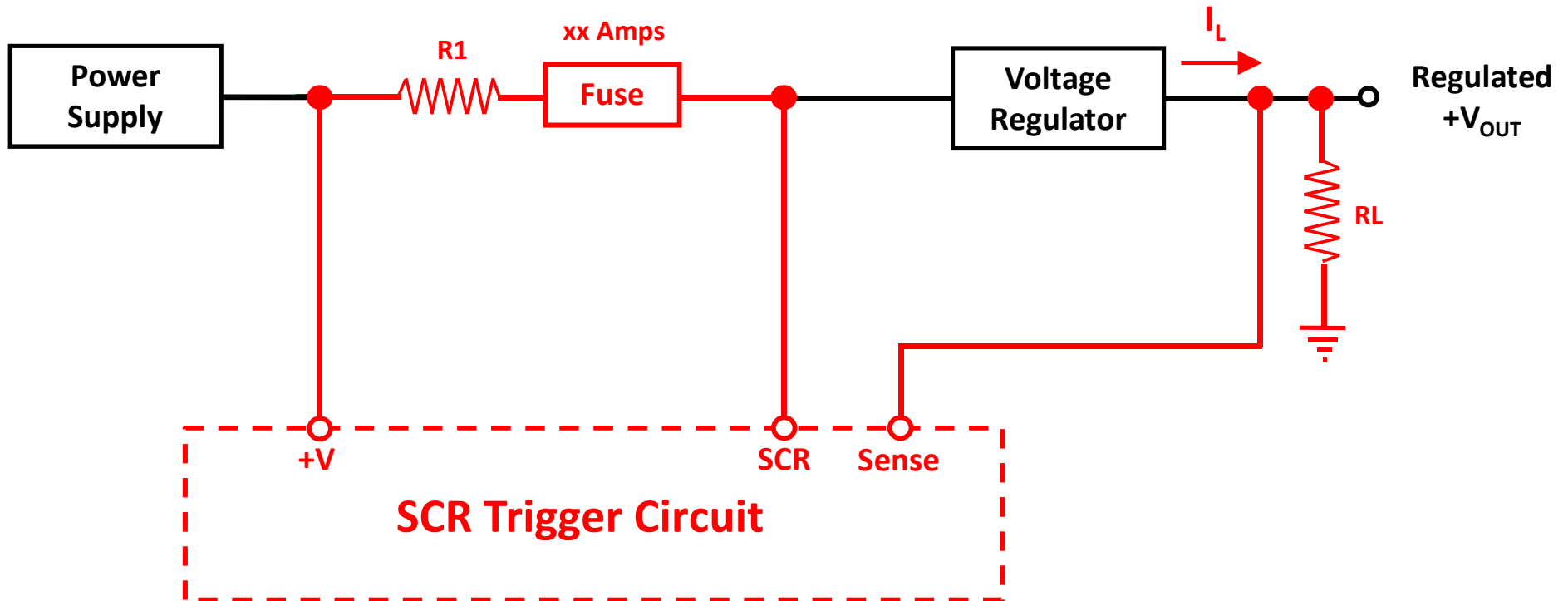


Problem 3: Most three terminal regulators must source 3-5 mA for regulation to occur

Overvoltage Protection Circuit in ARRL Handbook

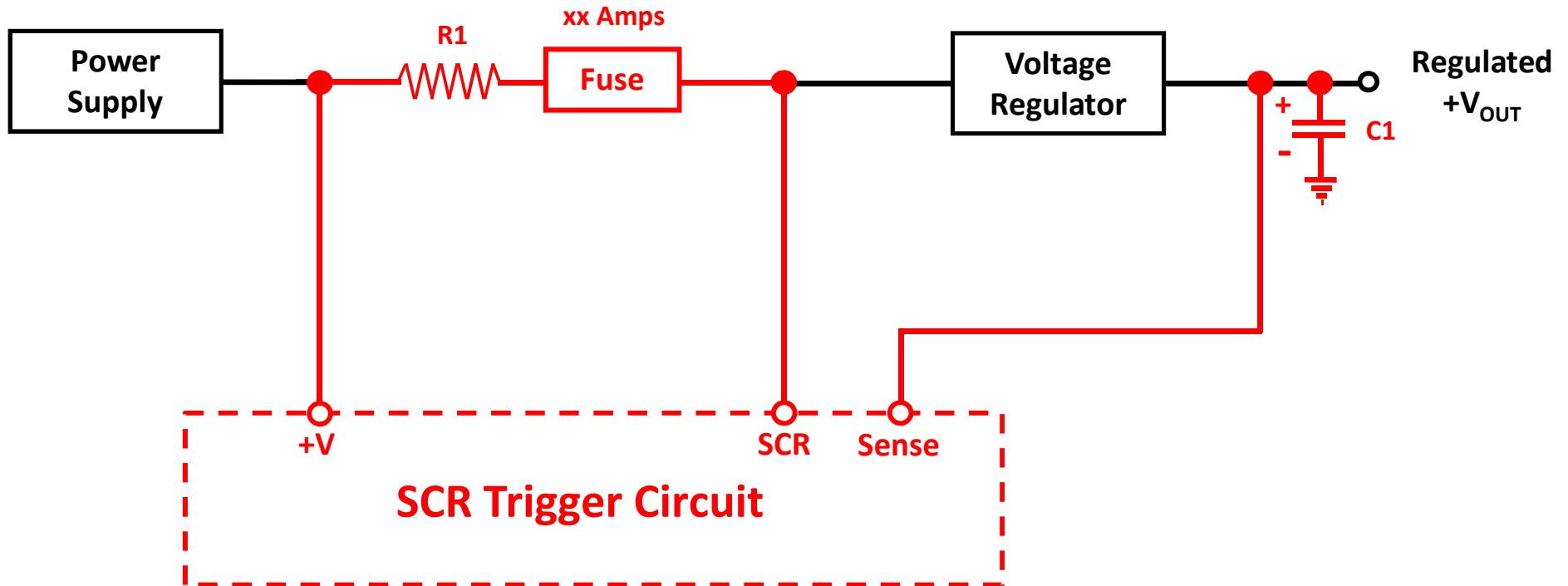


Problem 4: Most three terminal regulators should be protected from damage that could result from a short on the input

Overvoltage Protection Circuit in ARRL Handbook

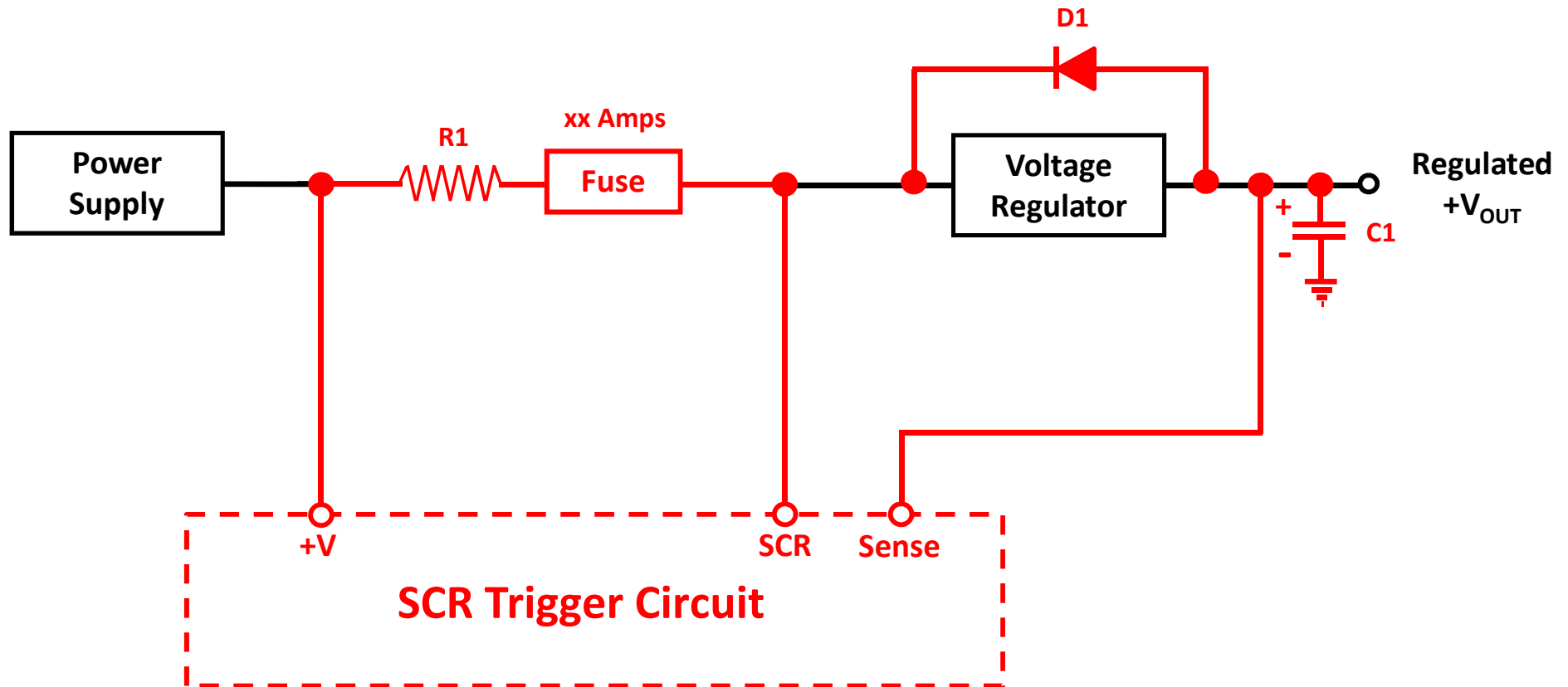


Problem 4: Most three terminal regulators should be protected from damage that could result from a short on the input

Overvoltage Protection Circuit in ARRL Handbook

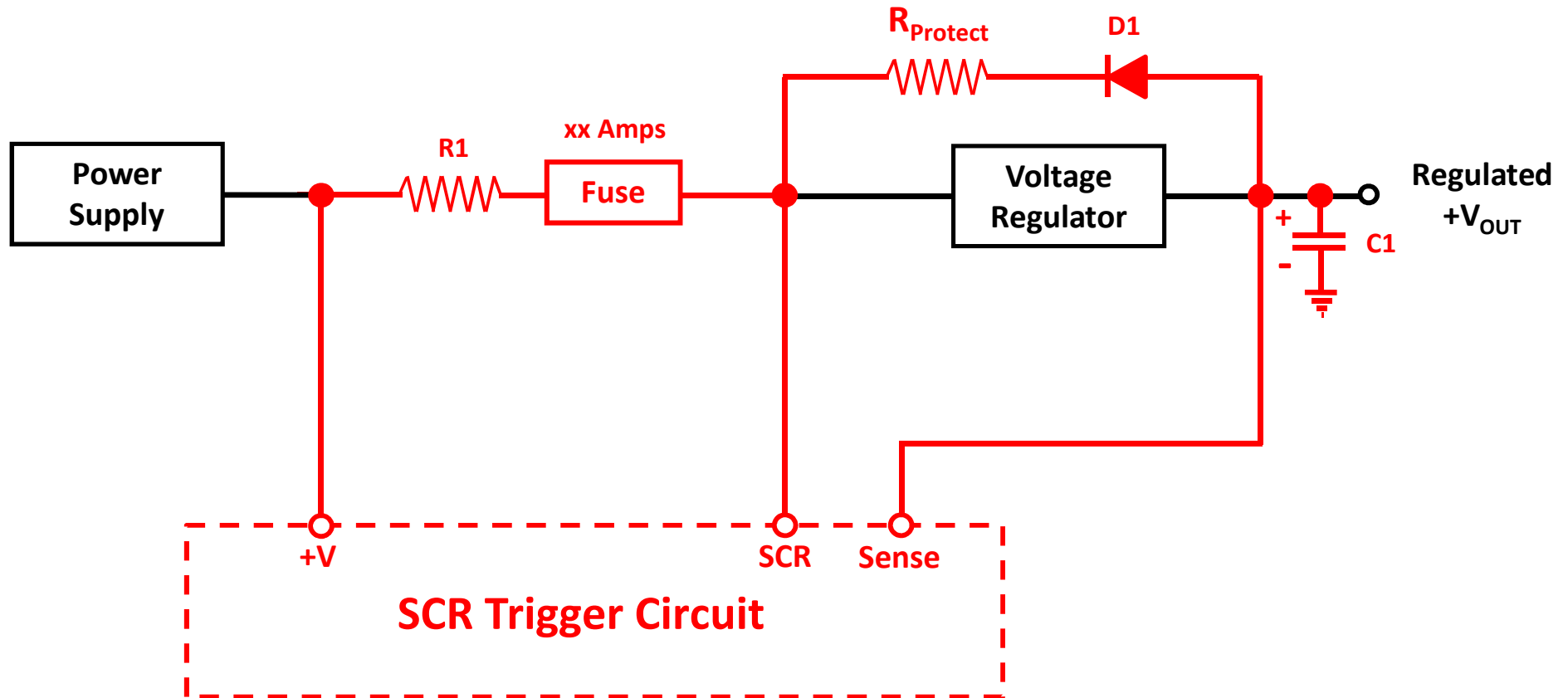

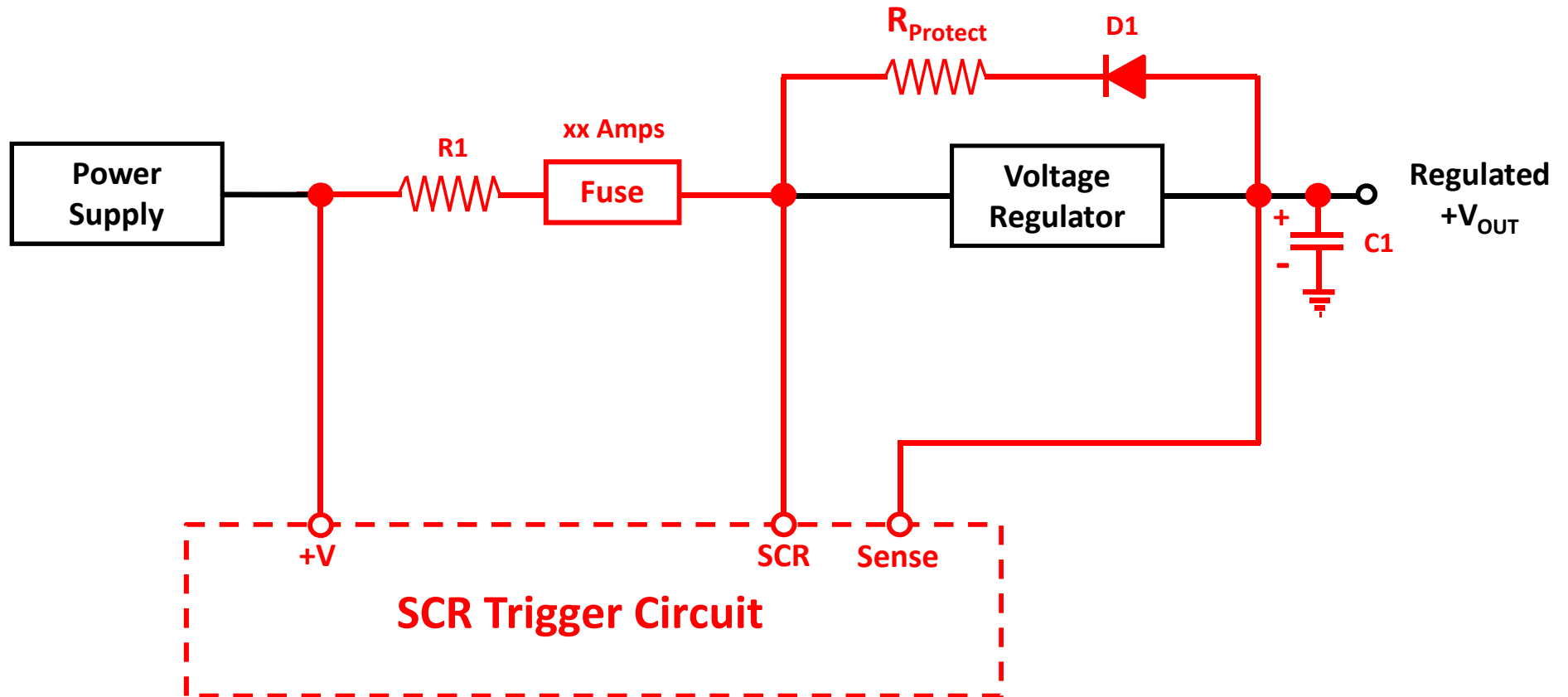Problem 4: Maximum current through D1 should be limited whenever an overvoltage protection circuit is used

Overvoltage Protection Circuit in ARRL Handbook




Note: R1 & R_{protect} may need to be high wattage

- Don't want them to blow open when SCR fires


Solid Copper Wire

Wire Size	Fusing Current	Resistance
Gauge	Amps	Ohms/10 ft
26	20	0.408
24	29	0.257
22	41	0.161
20	58	0.102
18	83	0.064
16	117	0.040


Modified Overvoltage Protection Circuit

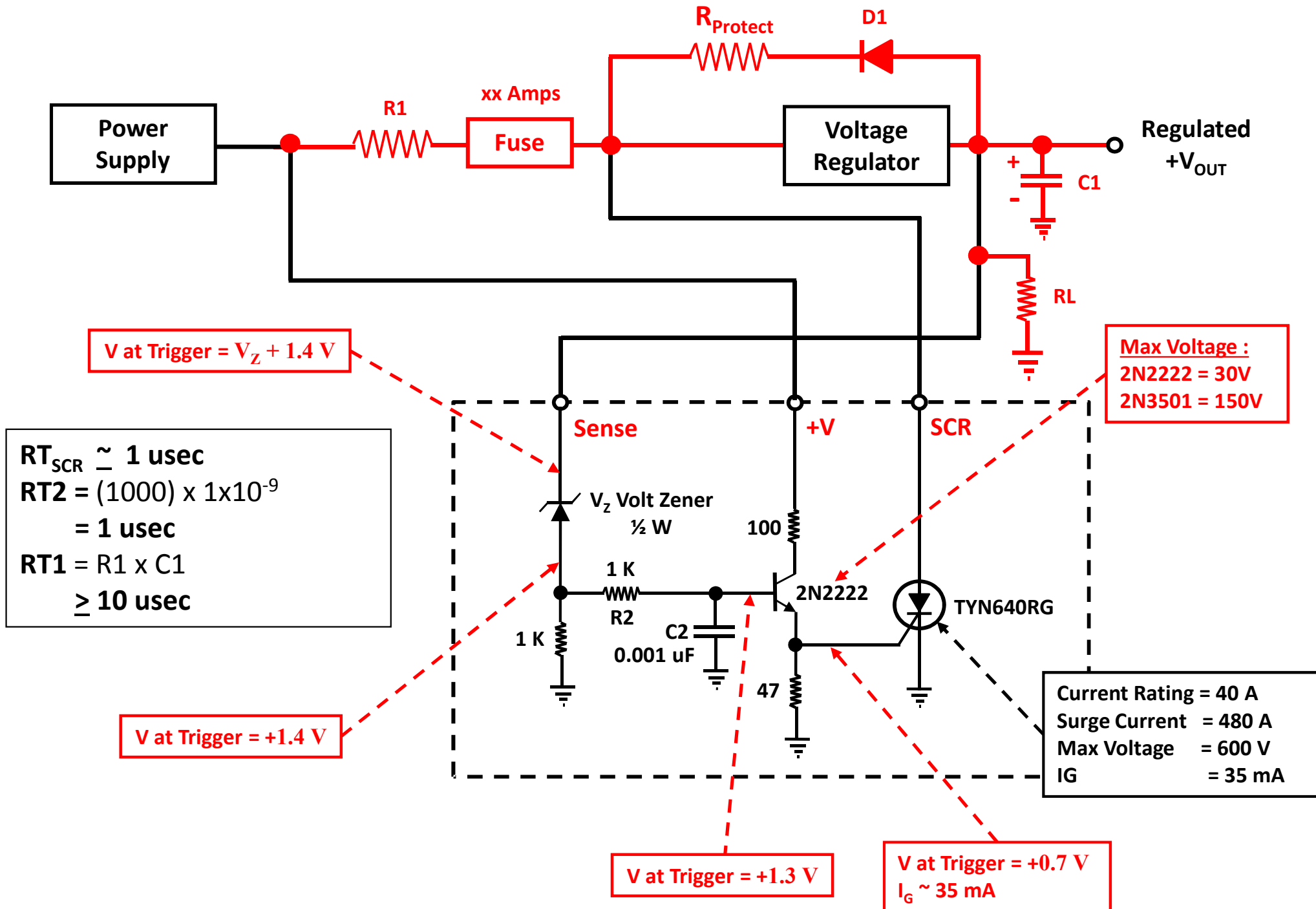

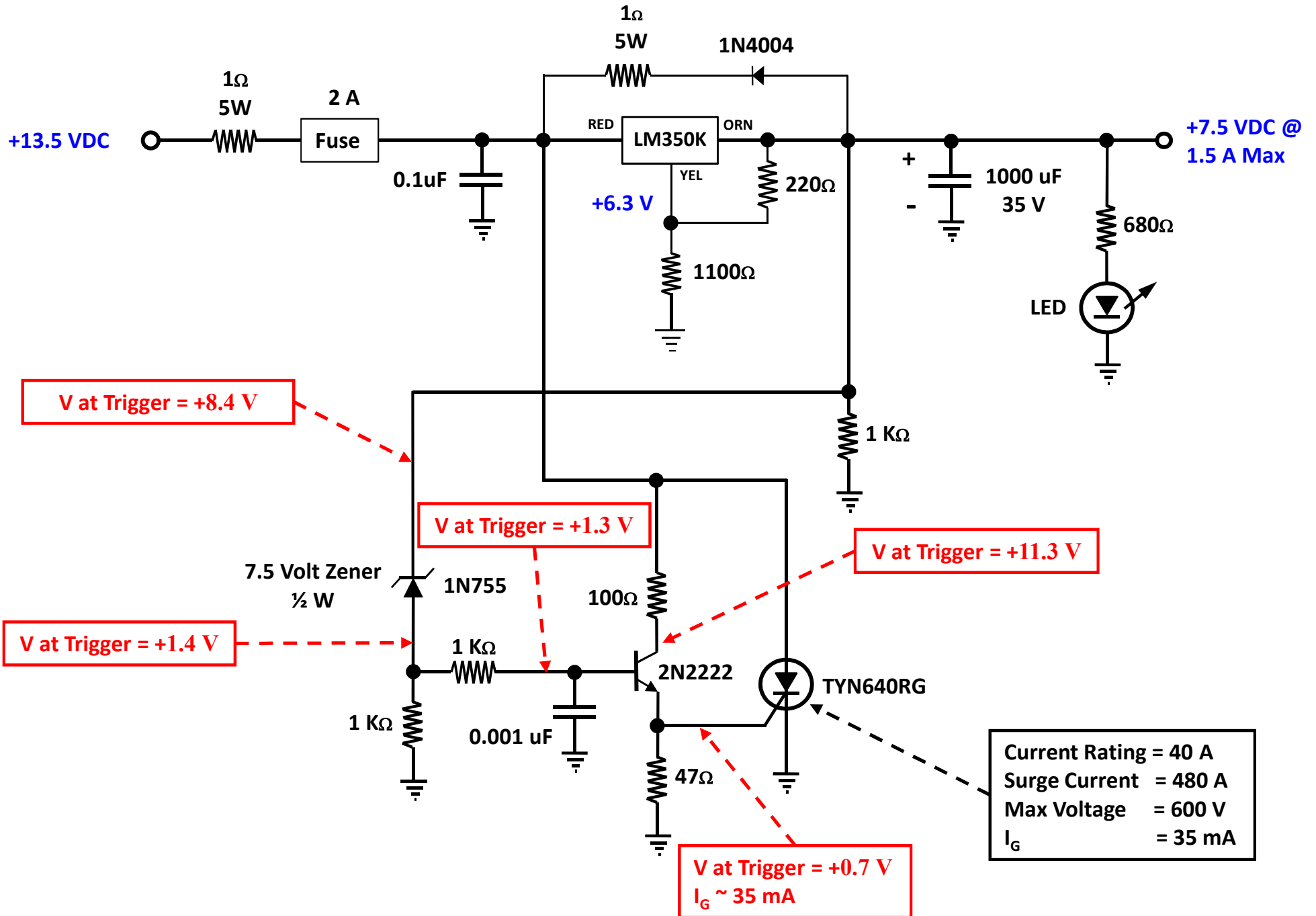
ICOM V80 Power Supply With Overvoltage Protection



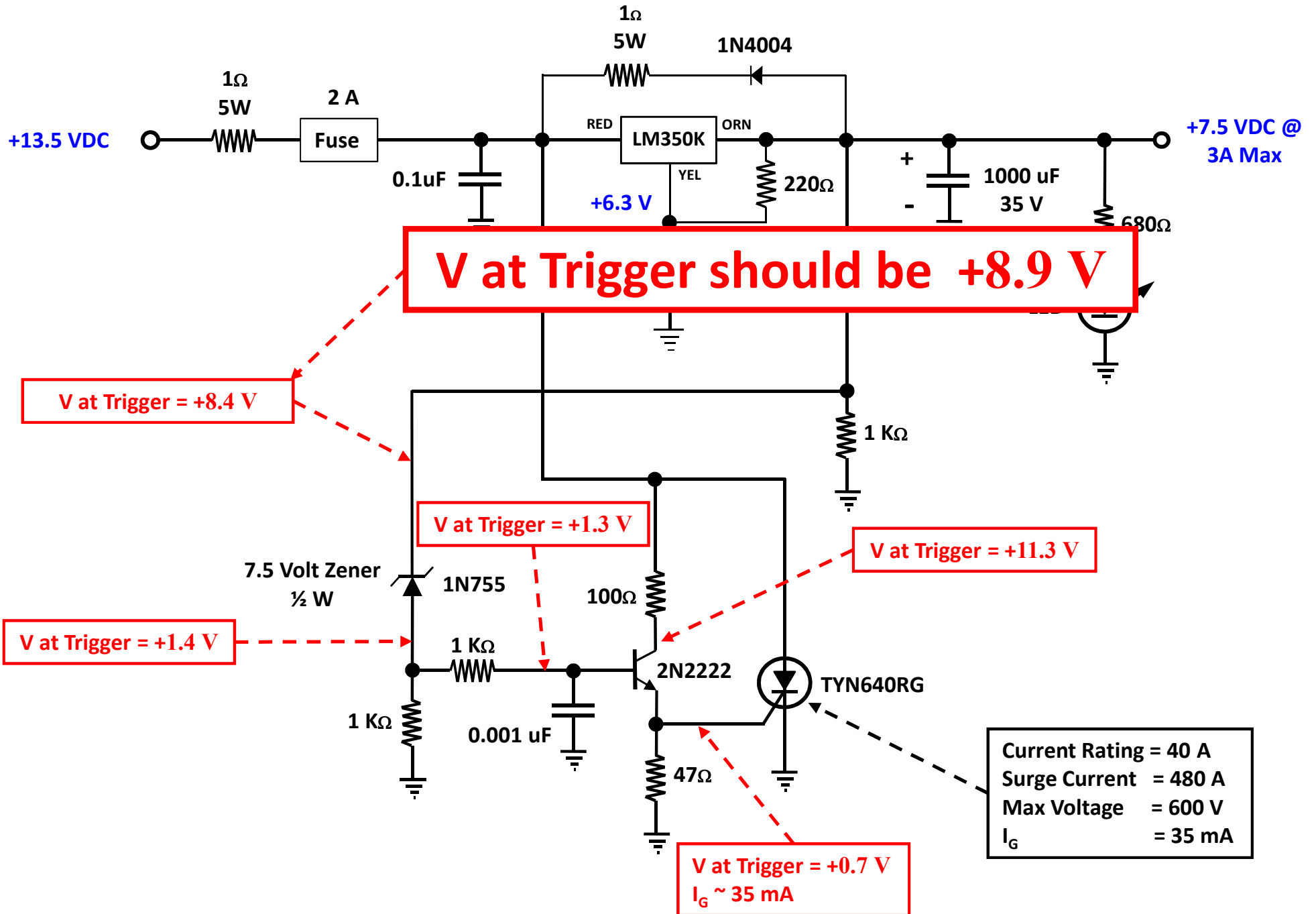ICOM V80 Power Supply With Overvoltage Protection



Zener Diode Characteristics

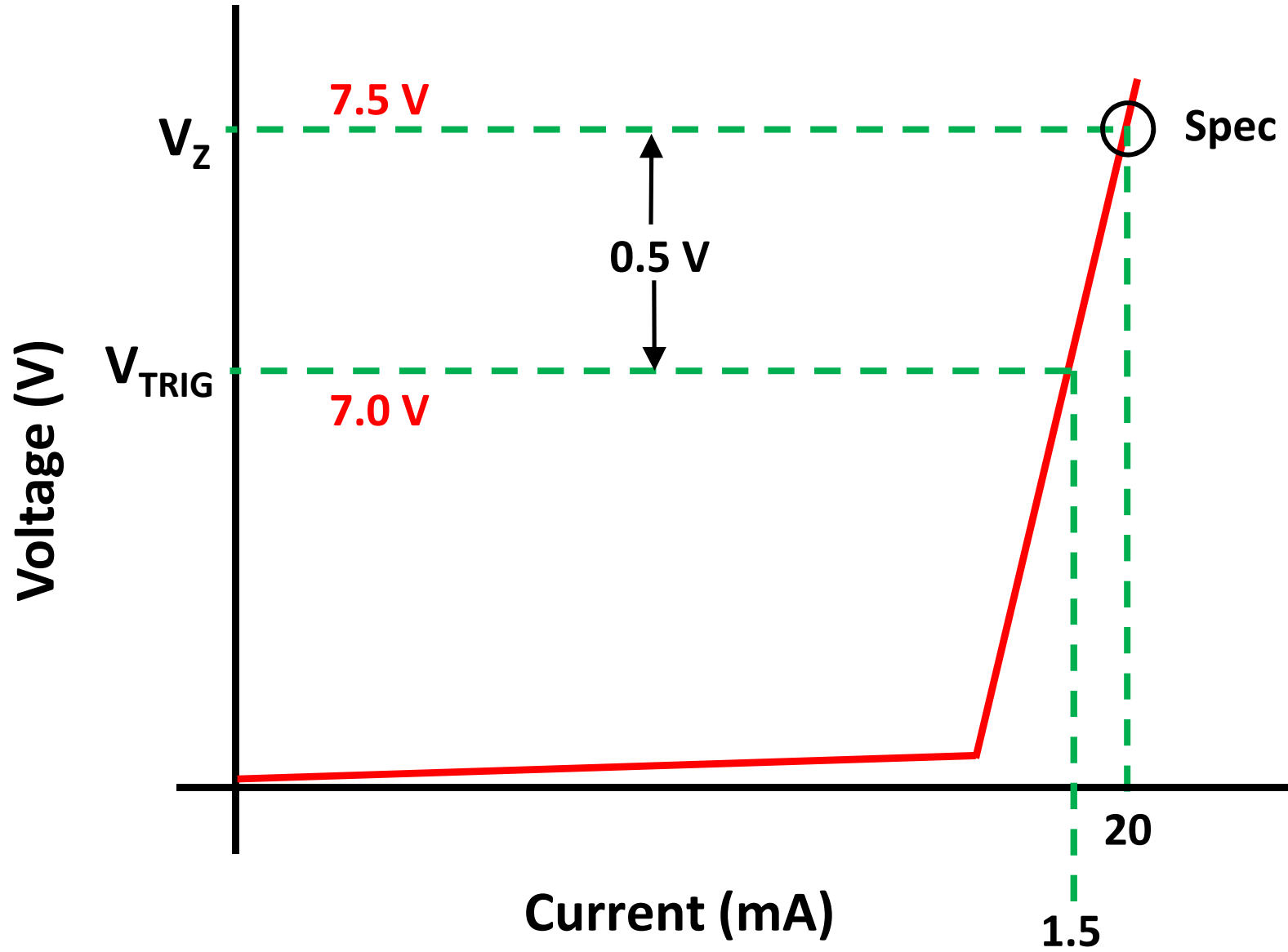

Check your SCR after installation!!!!