

Got Match?

Bill Leonard NØCU

Rev A

NAØTC - 285 TechConnect Radio Club

<http://www.naøtc.org/>

Frequently Asked Questions:

1. What is meant by “Match”?
2. When should I use an Antenna Tuner?
3. Where should I place the Antenna Tuner?

What is meant by “Match”?


- To achieve a “Perfect Match”, we need to simultaneously achieve two different types of match:
 - **Z_0 Match**
 - Drives the selection of **Source, Load, and Transmission Line impedances**
 - To achieve minimum loss, SWR must equal 1:1 on all transmission lines
 - **Conjugate Match**
 - Defines conditions for maximum power transfer from Source to Load
 - This is usually what is meant when the term “Match” is used

Good reference: “Reflections III” by Walter Maxwell (W2DU)

Why Do We Want a “Perfect Match”


A “Perfect Match” results in the:

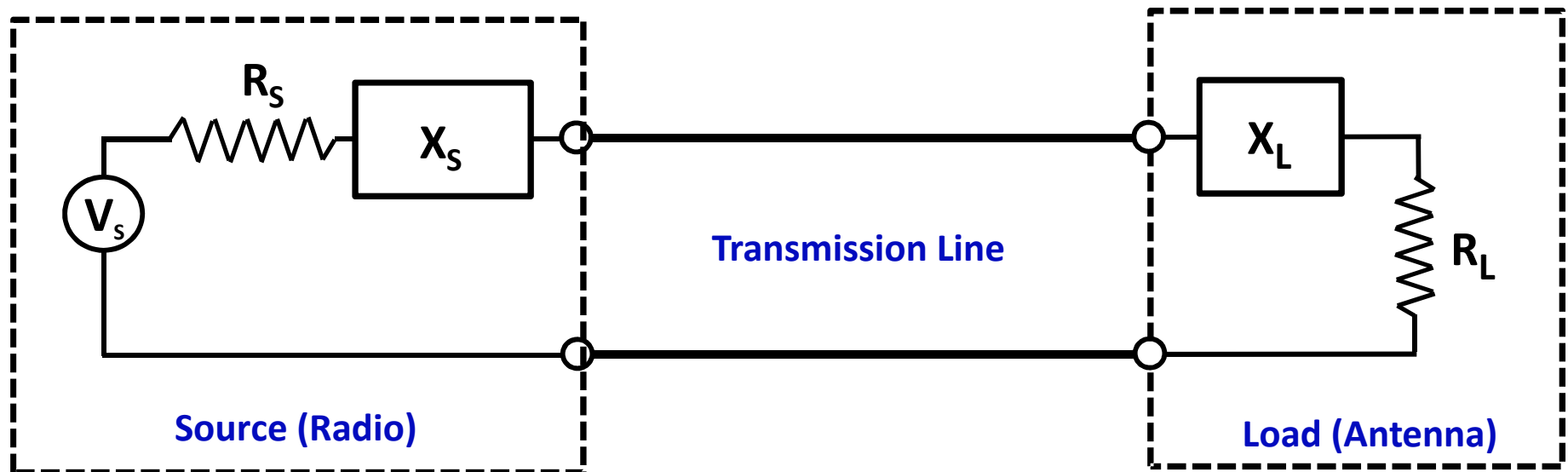- 1) **Maximum Available Power** being generated by the Source
- 2) **Maximum Available Power** being absorbed by the Load
- 3) **SWR = 1.0:1** at any point in the “Antenna System”
- 4) **Wider operating bandwidth**
- 5) “System” (*not the antenna*) being tuned to resonance




What Is Meant By “Antenna System”?

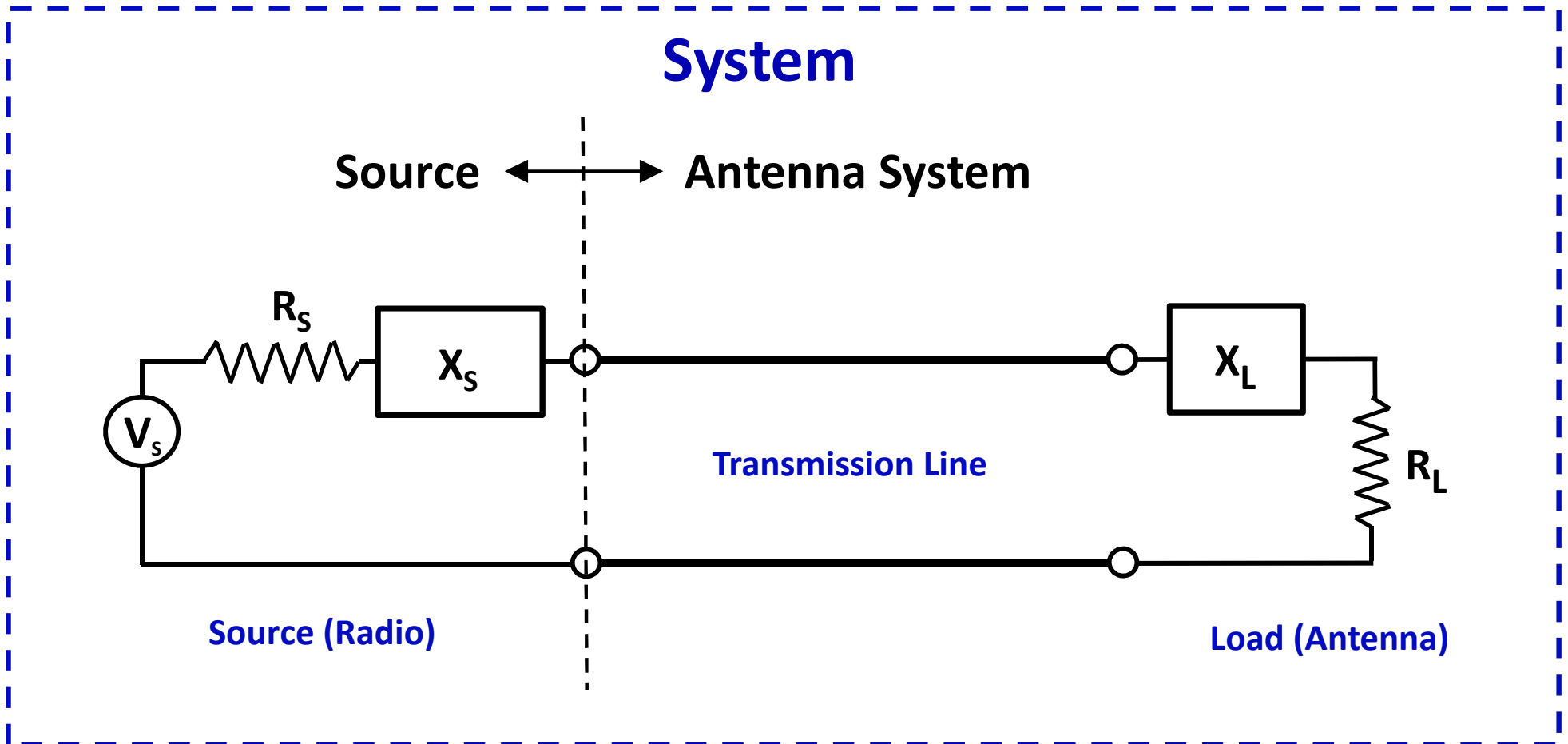- The “System” includes all hardware from the the Source, thru the Load



What is a “ Z_o Match”?

- Z_o = Characteristic Impedance of a Transmission Line
 - $Z_o = R_o + jX_o = R_o + j\cancel{\square} = R_o$ (for most Ham applications)
- “ Z_o Match” is achieved when the impedance seen by a transmission line, at each end of the line, is equal to the impedance of the line (Z_o):
 - Simply stated: $Z_s = Z_L = Z_o \cong R_o$
 - For cases where there is no reactance:
 - Z_o Match = Perfect Match
 - No need for an Antenna Tuner

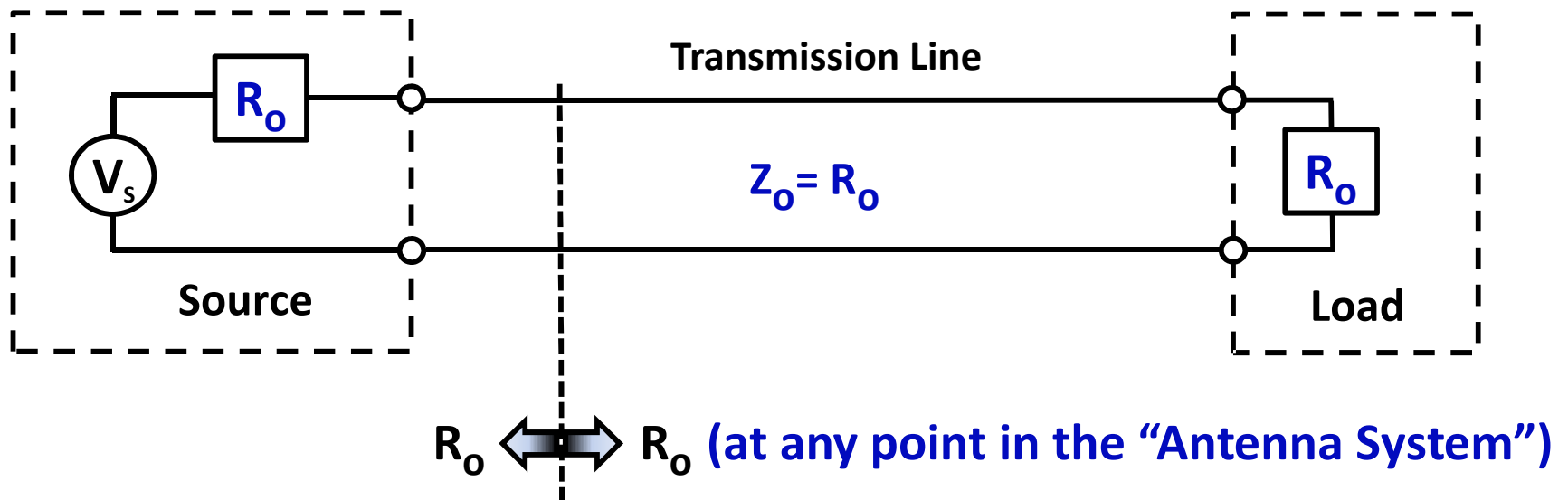

What is a “Conjugate Match”?

- Two conditions must be met (at any point in the “System”)

1) $R_{\text{Left}} = R_{\text{Right}}$

2) Net Reactance in the “System” = 0

- $jX_{\text{Left}} = -jX_{\text{Right}}$
- “System” is resonant



$$Z_{\text{Left}} = R_{\text{Left}} + jX_{\text{Left}} \longleftrightarrow Z_{\text{Right}} = R_{\text{Right}} + jX_{\text{Right}}$$

Note:


1. “Conjugate Match” is independent of the Transmission Line
2. For cases where there is no Transmission Line:
 - **Conjugate Match equals a Perfect Match**

How To Achieve A “Conjugate Match”?

•Typically:

• $Z_s = Z_o = 50 \Omega$ (not required) and,

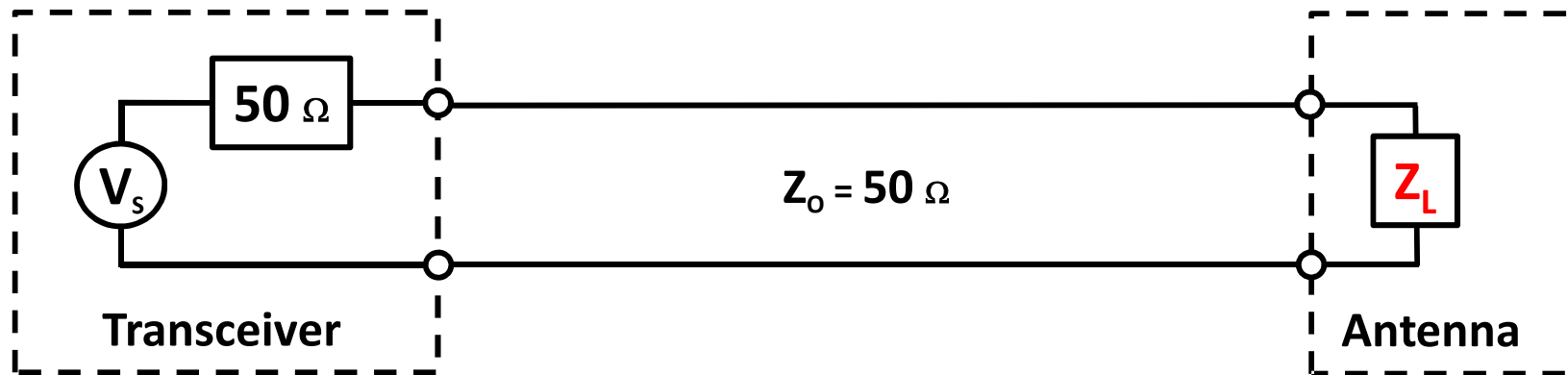• $Z_L = R_L + jX_L \neq 50 + j\boxed{} \Omega$




$$Z_L^* = R_L - jX_L \longleftrightarrow Z_L = R_L + jX_L$$

* => Conjugate

How To Achieve A “Conjugate Match”?

Use an Antenna (System) Tuner:

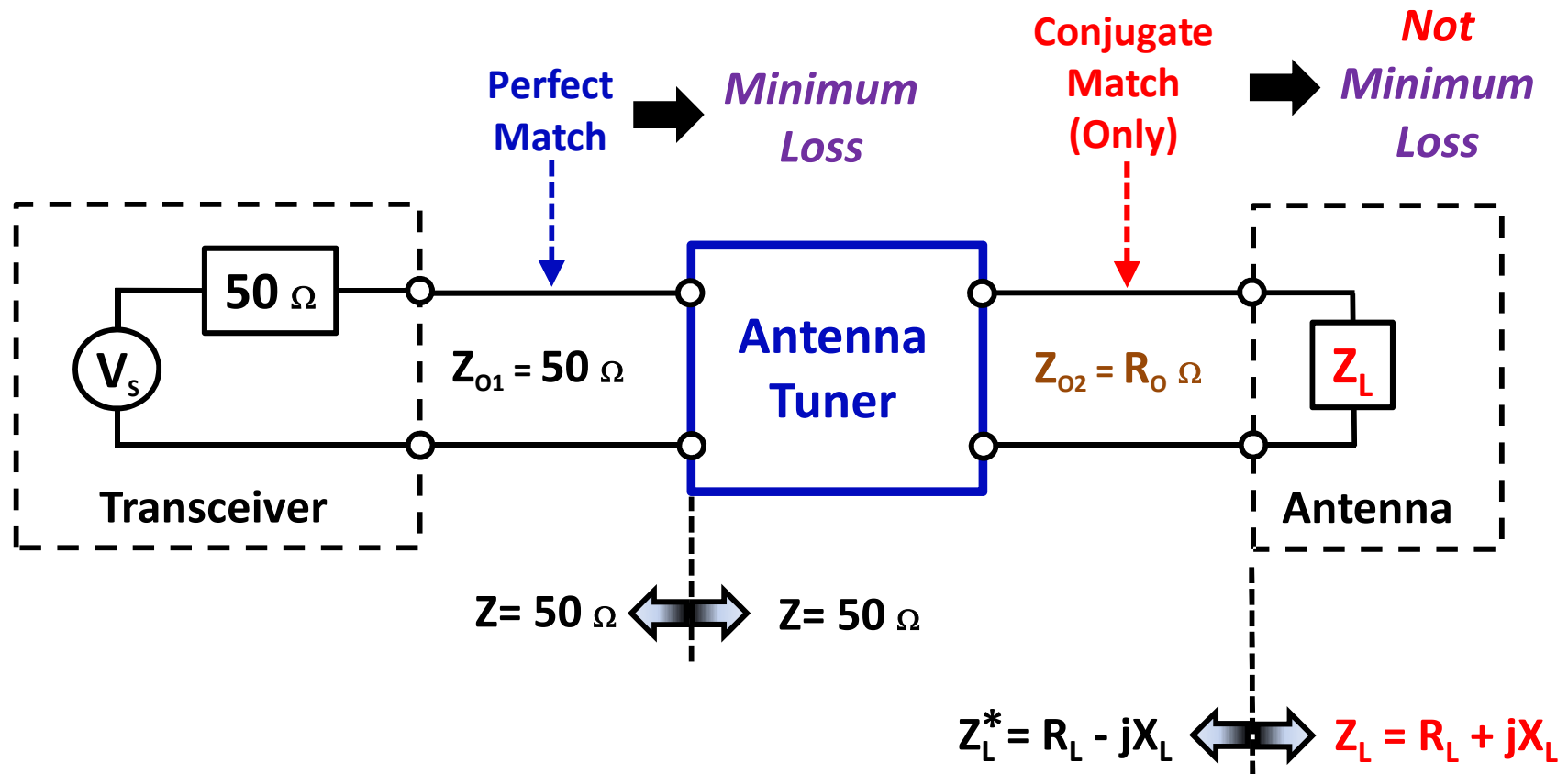


•Note: the “System” (not the antenna) has been “tuned” to resonance

How To Achieve Minimum System Loss?

Place the Antenna (**System**) Tuner at the Load:

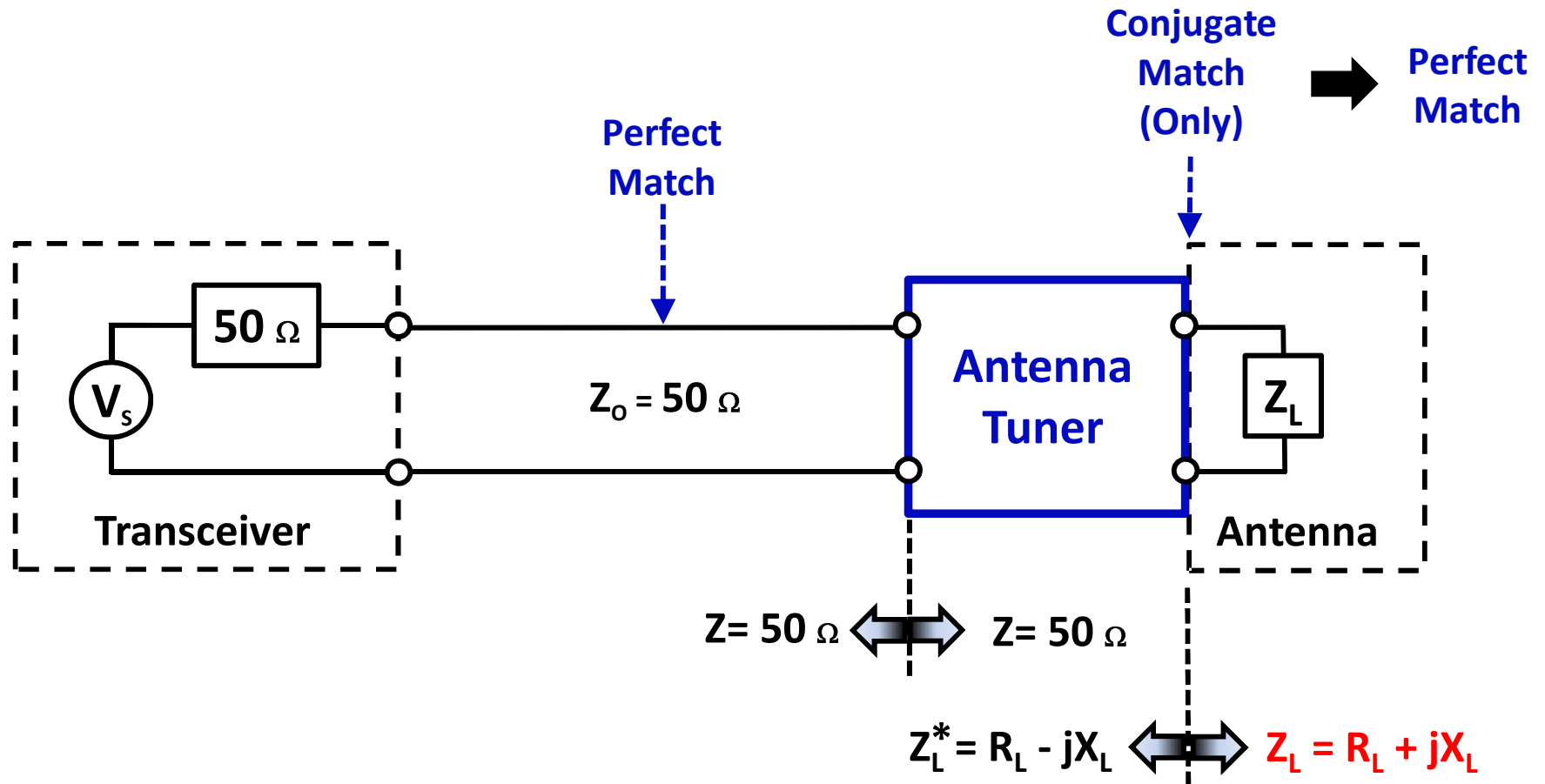- We now have a “Perfect Match” at all points in the “Antenna System”



Answers to “When” & “Where”

When:

1. The NET “System” loss can be reduced by more than the insertion loss of an Antenna Tuner
2. The SWR of the Load is high enough to cause the transmitter output power to be reduced because the SWR protection circuit is being activated
 - Usually between 1.5:1 and 2.0:1
3. Increased operating bandwidth is needed

Where:

- As close to the antenna as possible, or
- Where convenient, and use low loss transmission line between the antenna and the tuner