

Kirchhoff's and Ohms Law

Larry Weinstein, KØNA

Electrical Safety


- Working on modern electronics is generally quite safe
- Exceptions
 - High powered amplifiers
 - 2,000 to 4,000 Volts
 - Tube type equipment
 - Receiver voltages are typically 350 Volts
 - Transmitter voltages are typically 750 Volts
 - Power lines
 - 2 Killed a couple of years ago
 - **Three People Killed While Erecting Antenna (ARRL News letter)**
At approximately 8:40 PM on Monday, October 12, a man, woman and their 15 year old son were killed while trying to erect a 50 foot vertical antenna at the home of the man's mother, Barbara Tenn, KJ4KFF, in Palm Bay, Florida. The deceased were not licensed amateurs.
- Video

Kirchhoff's Law

- The sum of all the voltages around a loop equal to zero
 - You must go around the loop in one direction
 - The black lead is the reference voltage
 - The red lead is the measured voltage
 - The sum of the measured will equal zero
- Example: Skiing a loop
 - Height of the lift-sum of the drop of the trails back to the base=0
 - The altitude gained and lost in a complete loop is zero
 - Voltage (potential difference) is equivalent to change in elevation


Ohm's Law

- Voltage = Current X Resistance

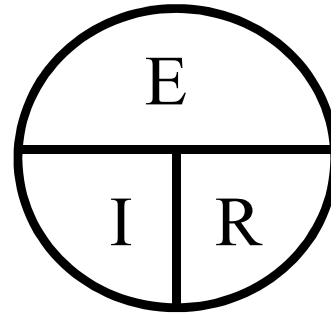

- Cover the unknown to get the formula


- Power = Volts X Current

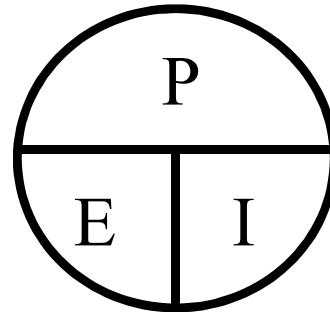

Application

Charging a 7.2 volt NiMD battery pack

- Rated at 2,000 ma-hr
 - Charge at $.1 \times 2,000 = 200\text{ma}$
- Power supply is 13.8 Volts
- Kirchoff's law
 - Power supply + resistor+diode+battery=0
 - $13.8 - V_{\text{resistor}} - .6 - 7.2 = 0$
 - Resistor voltage = 6 Volts
- Ohm's law
 - Resistance = $6 \text{ volts} / .200 \text{ Amps} = 30 \text{ Ohms}$
- Power on the resistor
 - Power = $.2 \text{ amps} \times 6 \text{ Volts} = 1.2 \text{ Watts}$

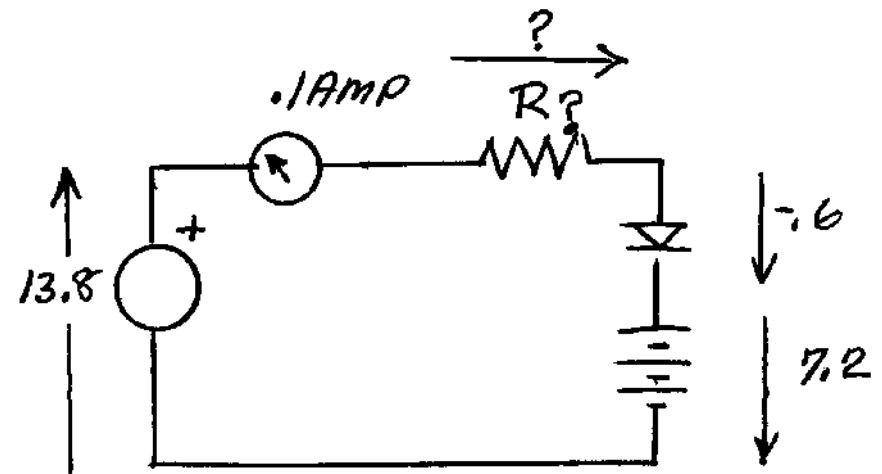

Options


- A 33 Ohm 1.5 Watt resistor
- 3 10 Ohm .5 Watt resistors in series
 - $R_{\text{total}} = R_1 + R_2 + R_3$
- 3 100 Ohm .5 Watt resistors in parallel
 - $1/R_{\text{total}} = 1/R_1 + 1/R_2 + 1/R_3$
 - On a calculator the key strokes are:
 - $100 (1/x) + 100 (1/x) + 100 (1/x) = 1/x$ Your answer = 33.3
- Test the circuit !

Assumptions

- Battery voltage is 7.2
- No resistance in the amp meter
 - An ideal amp meter has zero resistance
 - What happens if we forget to change the scale and try to measure voltage
 - Video
- No resistance in the power supply
 - Check the battery eliminator in the next example

Using a Battery Eliminator

- Specifications
 - Output 9 Volts
 - Current 200 ma
- Open circuit voltage
 - 14.2
- Voltage with a 100 Ohm load
 - 11.1
- Internal resistance
 - Current in the 100 Ohm resistor = $11.1 / 100 = .111$ Amps
 - Voltage drop internal = $14.2 - 11.1 = 3.1$ Volts
 - Resistance internal = $3.1 \text{ volts} / .111 \text{ Amps} = 27.9$ Ohms
- Current into the battery with no resistor
 - Internal voltage drop = $14.2 - 7.8 = 6.4$
 - Current = $6.4 \text{ Volts} / 27.9 \text{ Ohms} = .229$ Amps or 229 ma

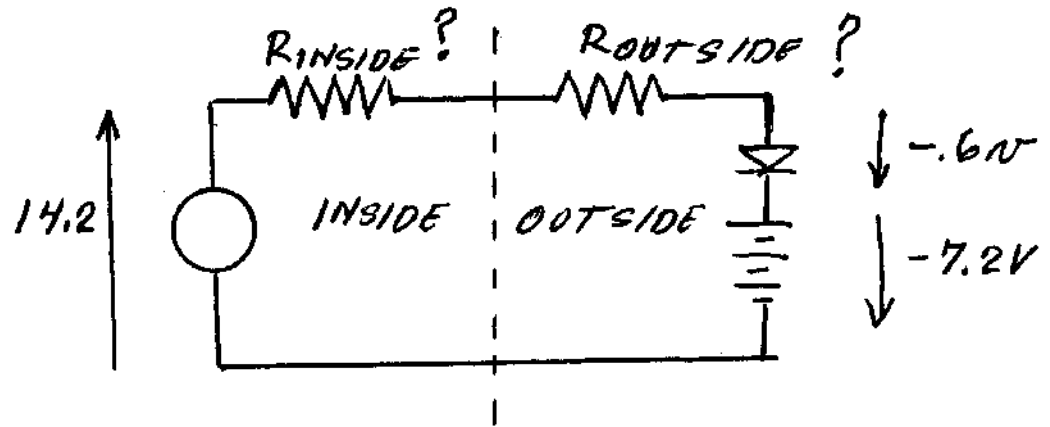

Volt Meters



- Ideal volt meter
 - Infinite resistance
- Real volt meters
 - Draw power from a circuit
- Potential problems
 - Can lower the measured voltage due to current draw
 - Example
 - Many schematics will specify a Ohms per Volt meter
 - Resistance equals the Ohms per Volt times the meter scale
 - For example 10,000 Ohms per Volt and the 100 Volt scale =1,000,000 Ohms
 - Some meters have a fixed resistance like 10 M Ohms

Capacitive Discharge

- Capacitors can hold a charge a long time
 - Extremely high currents are possible
 - Potential hazard
- Vaporized copper!
 - Example
 - The copper can keep an arc going a long time
 - In high power circuits it can coat eyes and skin!
 - In low power circuits it can plate out on the cold surface of a fuse leaving you with no protection!

Inductive Kick

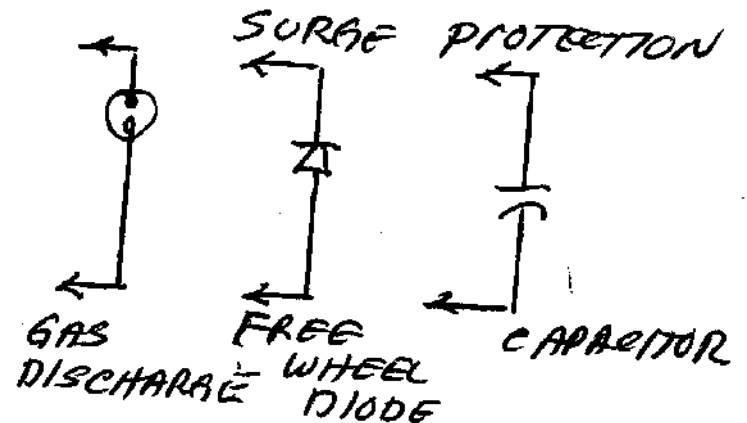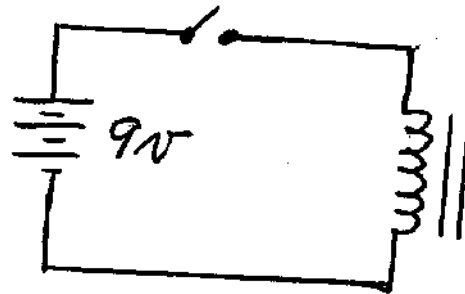- Inductance stores energy in a magnetic field
- Inductance tries to keep the current flowing
- Interruption of the current can create very high voltages that can damage equipment
 - Example
 - Typical failures:
 - mobile radios when you start a car
 - switching transistors feeding a relay



Questions