

Practical Tricks with Transformers

Larry Weinstein

KONA

Practical Tricks with Transformers

- Quick review of inductance and magnetics
- Switching inductive loads
- How many voltages can we get out of a \$10 Home Depot transformer
- Current transformers


Our Example Transformer

- We will use a Packard PF42440 120/208/240 to 24 volt transformer available at Home Depot on line for \$10 as an example.
- We will show how to get 32 different voltages from 12 to 264 volts from the transformer for a variety of applications.


No Load Characteristics

- If we look at a transformer with an open secondary it will look like an inductor.
- Reactance will equal $X = 2 * \text{Pi} * \text{Frequency} * L$
- Current will equal $I = \text{Volts} / X$


The Home Depot Transformer Connections

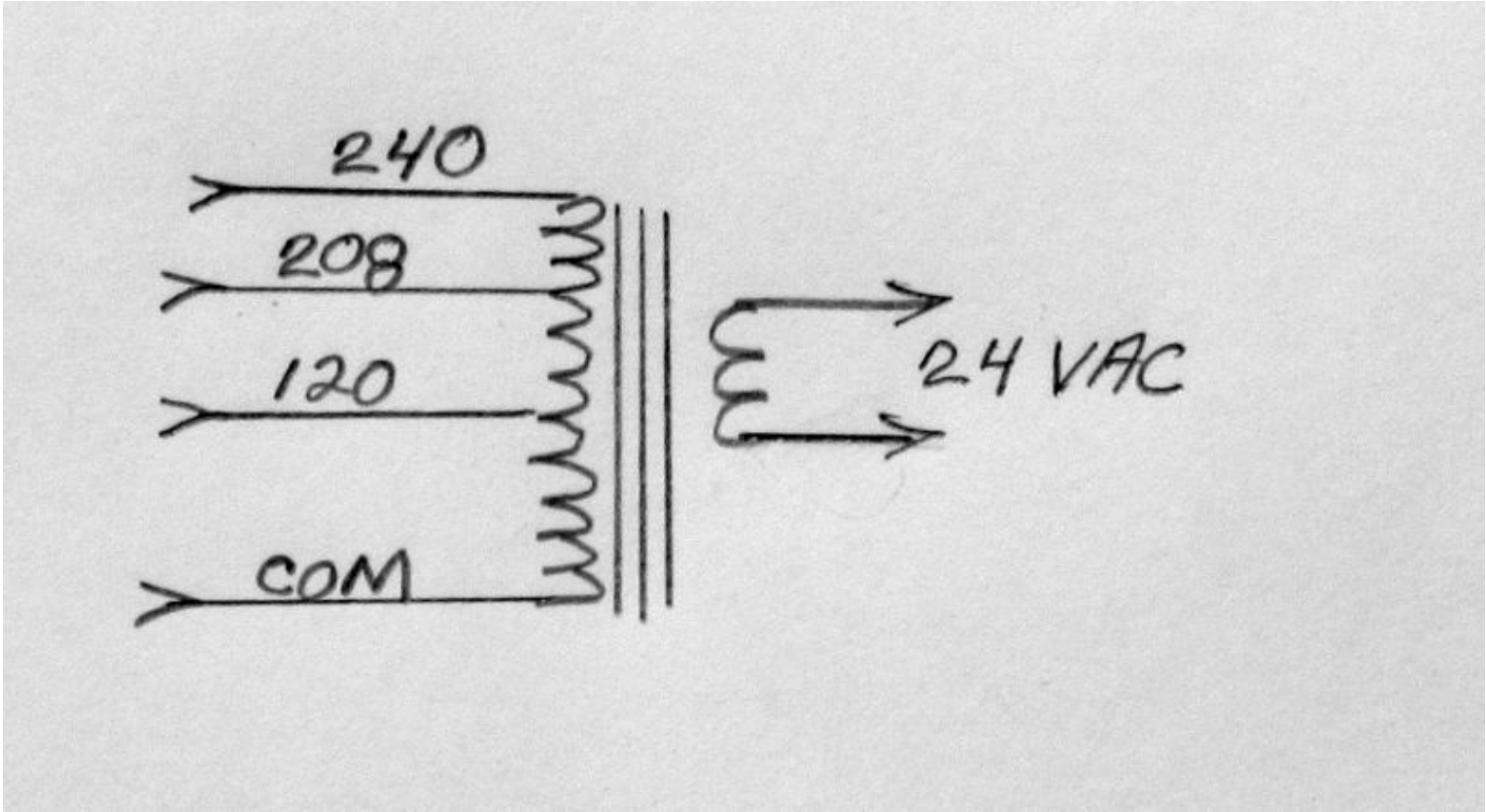

No Load Current vs Voltage

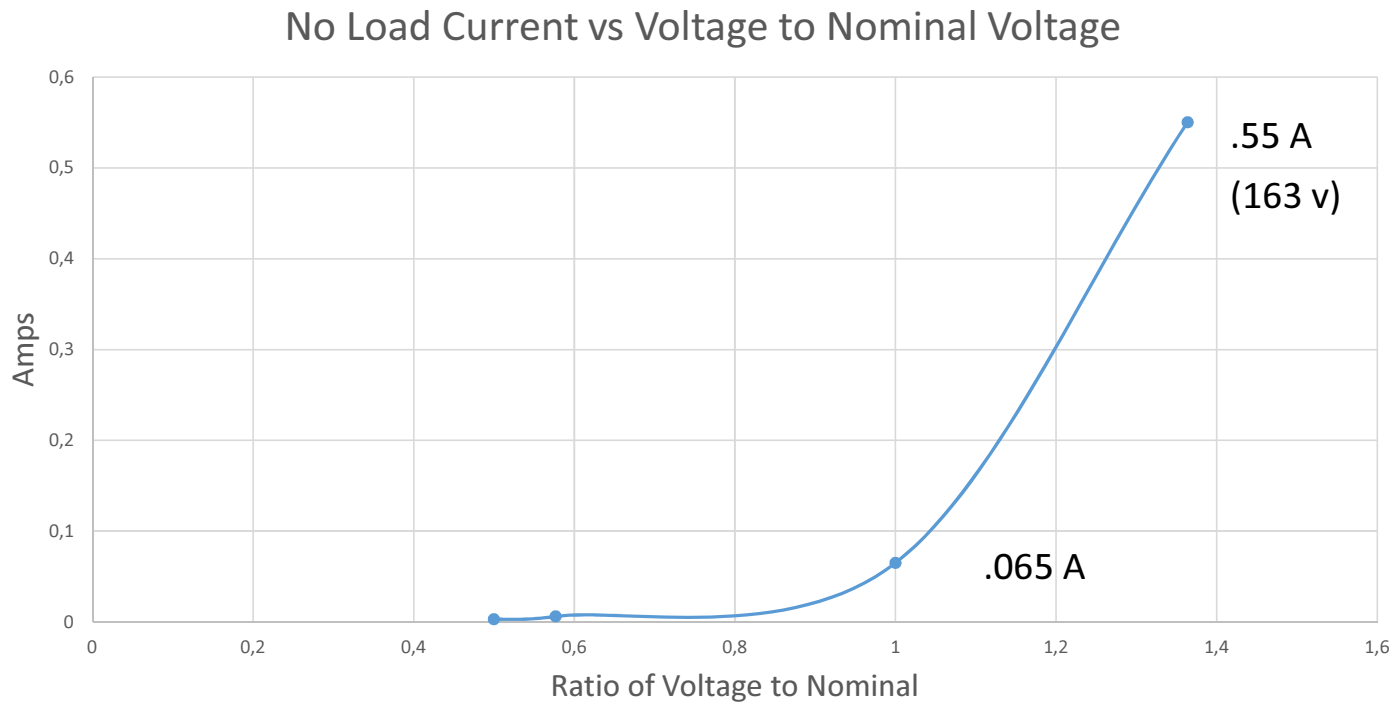

No Load Power vs Voltage

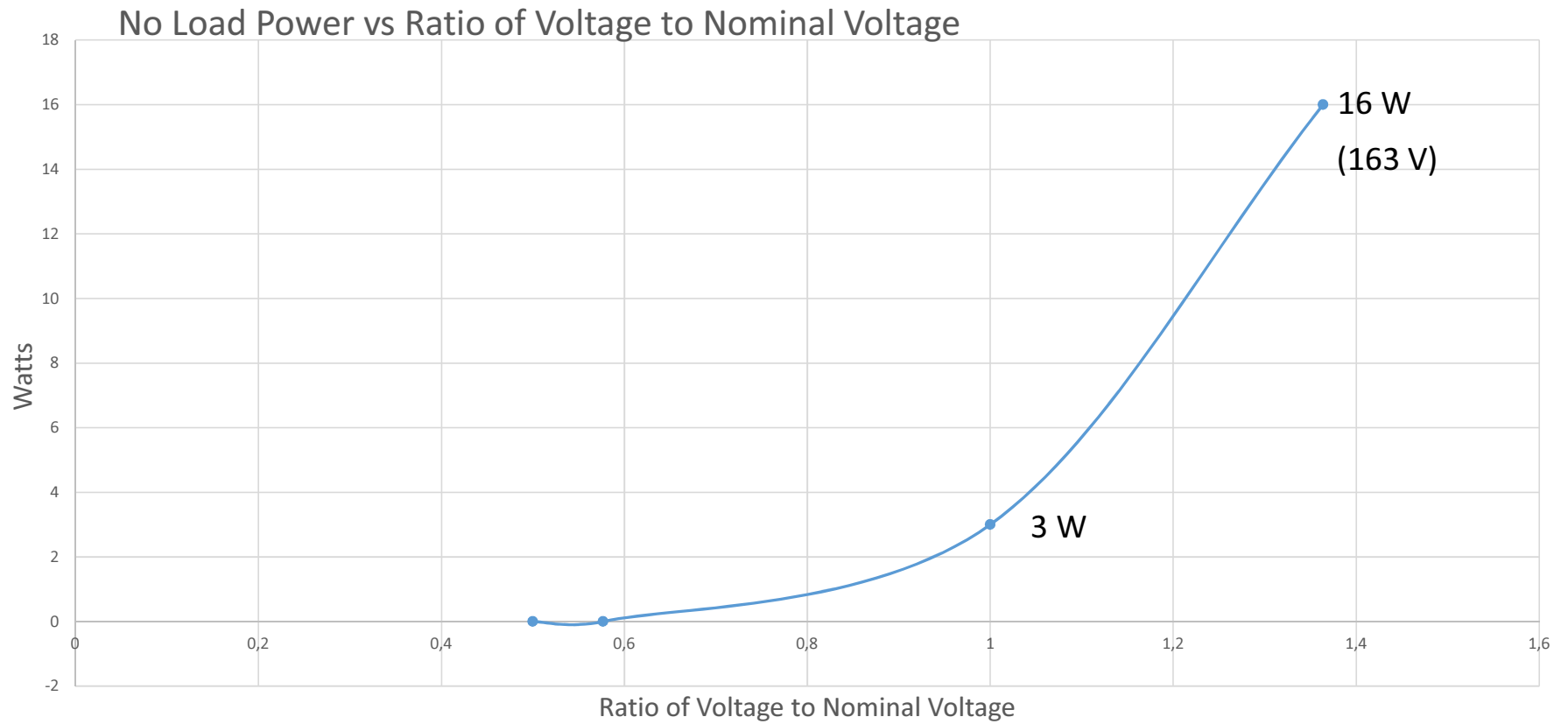


Practical Take Away

- I have an old radio rated for 110 VAC.
- My line voltage runs between 122 and 129 volts
- What can I expect from the transformer and life of the tubes?
- Would it pay to somehow reduce the voltage?

Why the Nonlinear Current and Power Curves?

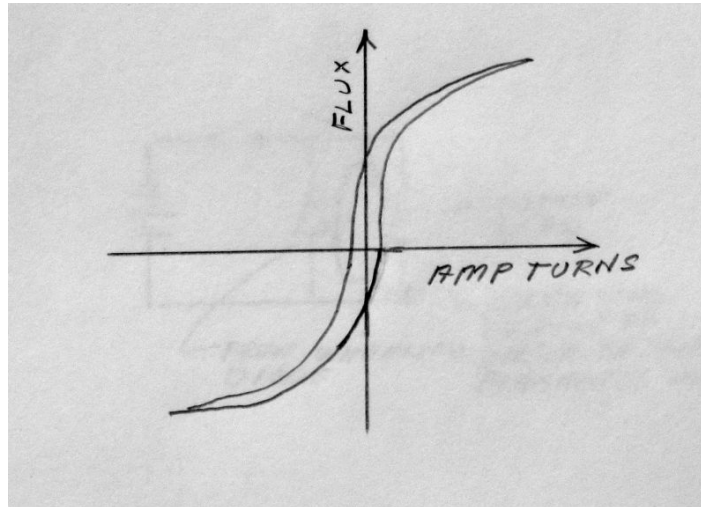- A typical curve of the magnetizing force vs magnetic flux for steel is nonlinear.



- | | | |
|--------------------|---|------------------|
| • Magnetic Circuit | | Electric Circuit |
| • Amps*turns | = | Voltage |
| • Flux | = | Current |
| • Reluctance | = | Resistance |
| • Permeance | = | Conductance |

More on Magnetics


- There is always a little residue magnetism left in the steel
 - This is the area in the center of the loop
 - This energy is lost each electrical cycle
 - Called hysteresis
- A voltage will be induced in a conductor to resist a change in flux
 - Example of the magnet in the tube
 - Called Eddy currents
 - The core is made up of laminated steel that has a blue insulating oxide finish
 - The laminations break most of the current paths with changing flux
- Enough energy must be stored in the magnetic field to replace the power put in the first part of the AC cycle
 - Remember no power is lost in a perfect inductor. Power is stored and returned during the cycle
 - If the frequency is doubled, only half the steel is needed

Magnetic Energy

- Magnetic flux is a form of energy
- In soft steel the flux can only exist with current (Except for a little hysteresis)
 - When an inductor is switched on, there is no field present and can draw very high currents to establish the field
 - The current called inrush can blow fuses
- When an inductor is switched off the field collapses
- The voltage in the each turn is proportional to the rate the flux changes therefore generating very high voltages to keep the current flowing till the energy is dissipated
 - Example with a coil and 4 NE2 neon bulbs (70 volts per bulb when firing)
 - What is the voltage on the 240 secondary?

Safely Switching Inductive Loads

- Free wheeling diode

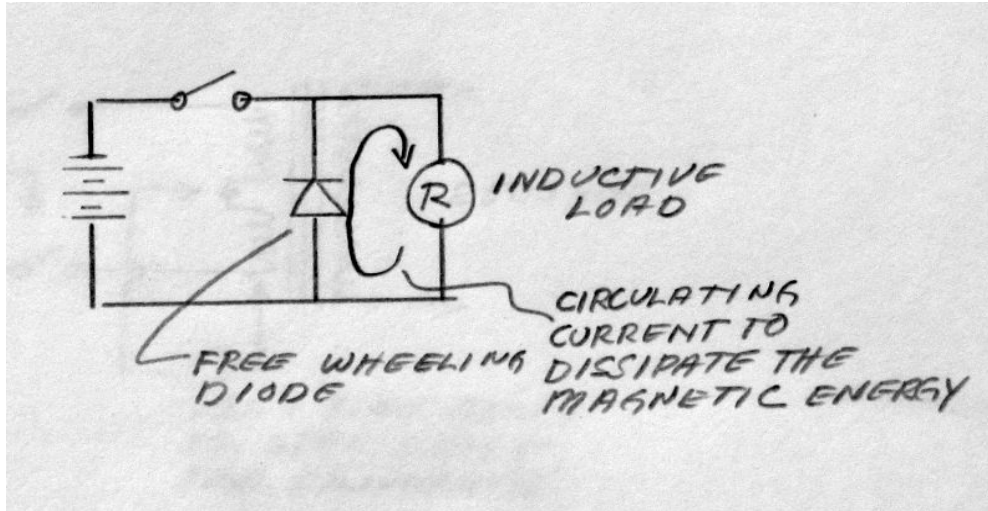

- Resistors, capacitors and surge protectors can also be used

Putting it All Together


- A voltage is generated in an inductor to match the applied voltage
 - The volts per turn is the same for any coil
- The voltage is the sum of the volts on each coil and the changing flux
- Flux is generated by the current through the inductor
- Enough current will be drawn to meet the flux requirements in the first statement
 - This known as the magnetizing current
- The maximum voltage on a transformer is a function of:
 - The amount of steel
 - The number of turns
 - Limited by the steel saturating

A Practical Moment

- Ignoring losses, the higher the frequency the less steel and copper is required
 - Less steel requires shorter coils
 - Less stored energy
 - Inductive reactance = $2 * \text{Pi} * \text{Frequency} * L$
- Aircraft uses 400 Hz AC. Weight = $60/400$ or .15 the weight of a 60Hz system
- A switching power supply running at 60KHz would be .001 the weight of a 60Hz system
 - Example 1 KW, 12 volt, 83 amp power supply

The Autotransformer

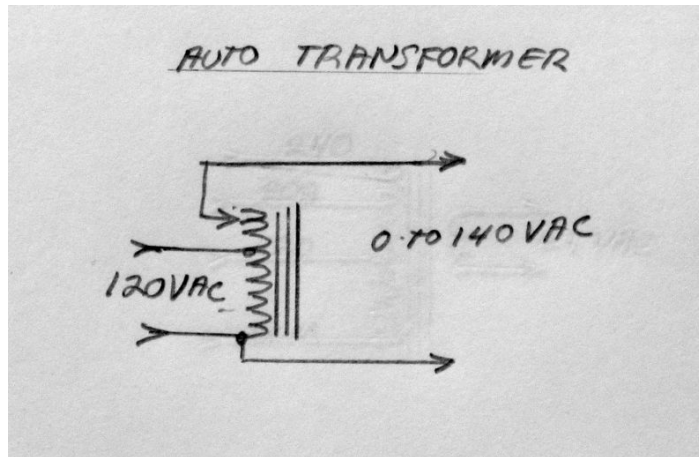
- The primary winding acts is also the secondary



- A variac is a an adjustable autotransformer
- The same can be done with fixed transformers


The Home Depot transformer

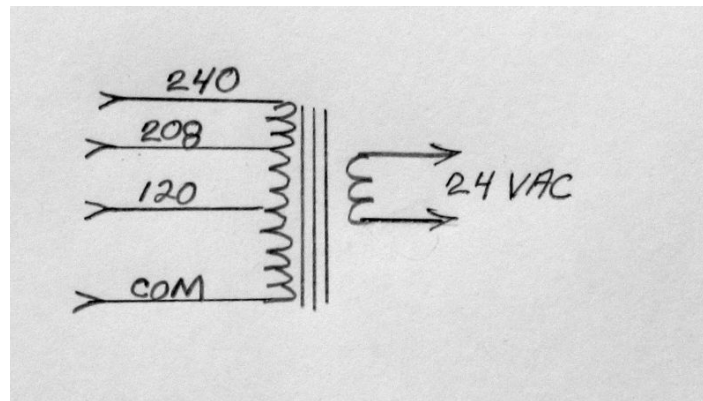- With 120 volts applied to the primary you will have 208 and 240 volts on the other 2 taps
 - The leads MUST be insulated
- With 240 connected to the primary you will have 120 and 208 volts available



A Practical Moment

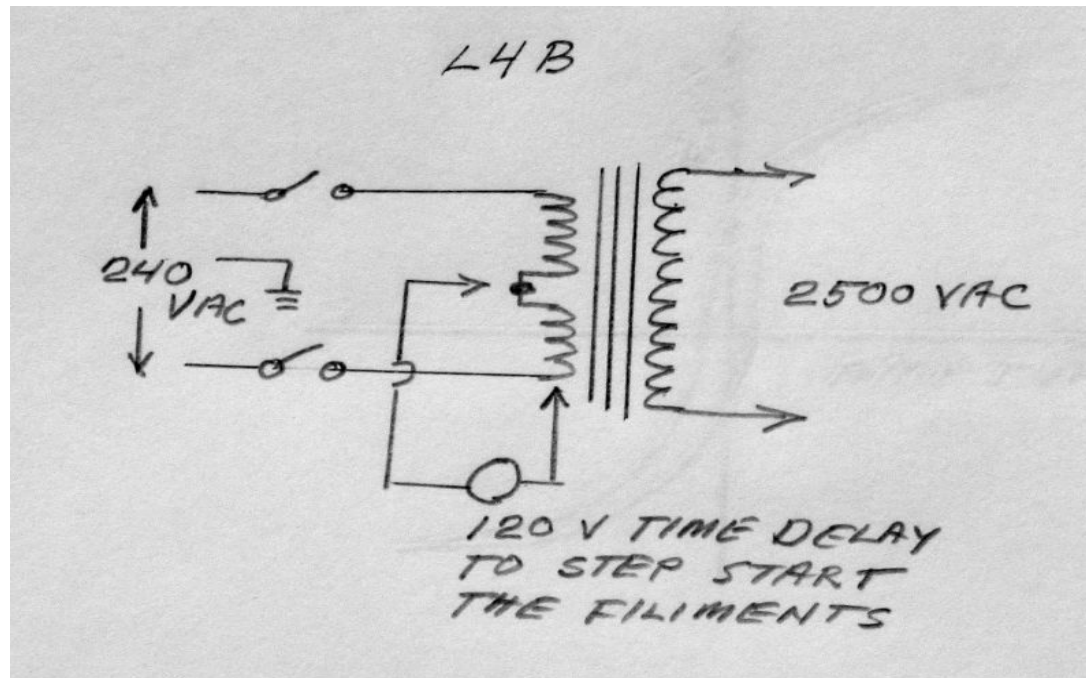- I have a 240 volt feed to the L4B amplifier and needed 120 volts for a step start timer
- Solution:




- I'll use the Home Depot transformer the same way to power the main 120 volt power relay in the new amplifier

Maximum Power and Current

- The transformer is rated for 40VA
 - VA is volts times current
 - VA is an optimistic estimate of power due to power factor
- Maximum current on a winding
 - Maximum current on the 24 volt winding is $40/24 = 1.66\text{A}$
 - Max on the 120 volt winding is $40/120 = .33\text{ A}$
 - Max on the 208 volt winding is $40/208 = .19\text{ A}$
 - Max on the 240 volt winding is $40/240 = 1.66\text{ A}$

Safe Limits for a Transformer

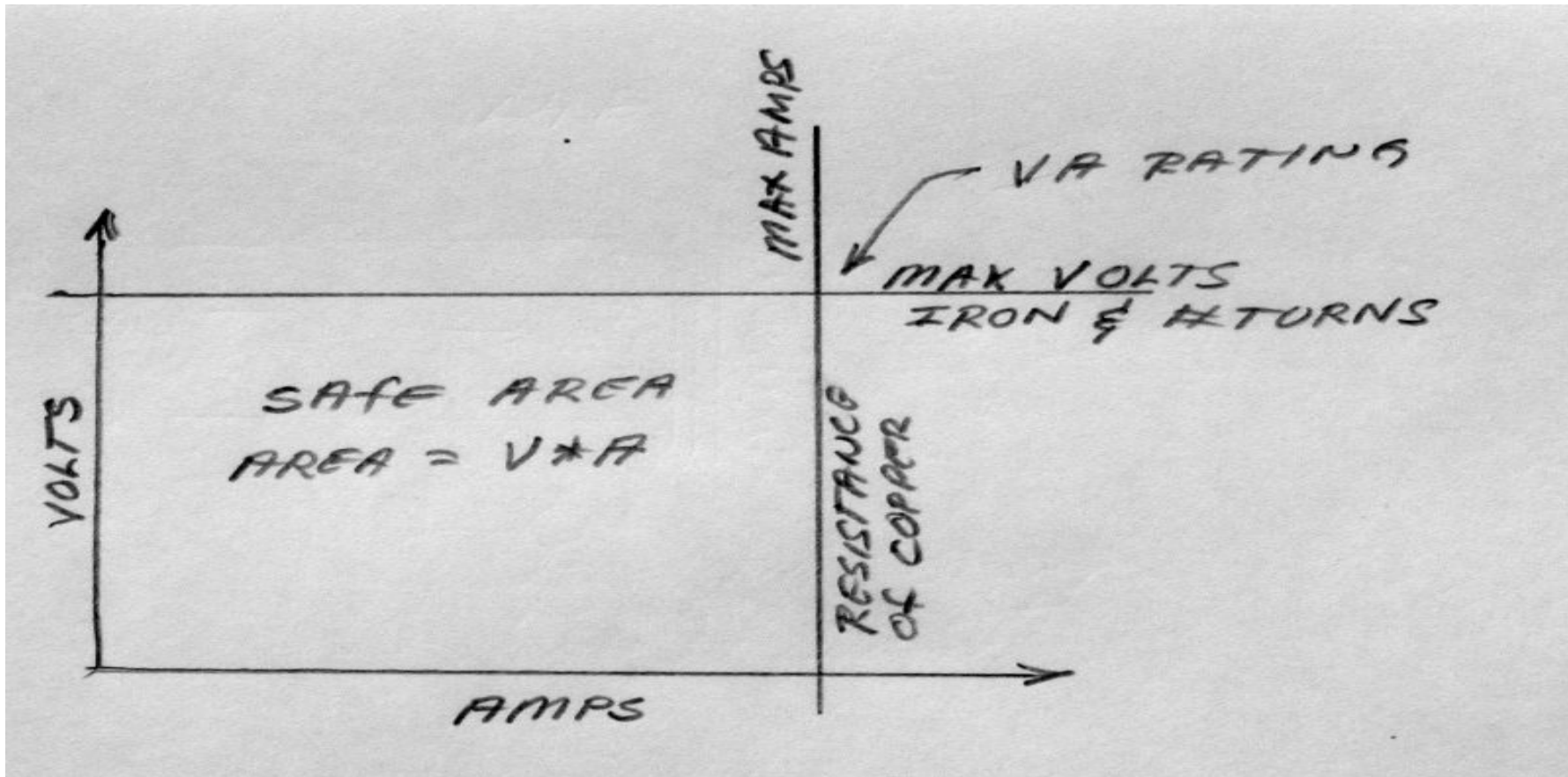

Voltage Possibilities

- 120 volts to the 120 tap
 - 24 V on the secondary
 - Plus the 208 and 240 volts on the primary
- 120 volts to the 208 tap
 - 13.8 V ($120/208*24$)
 - Plus 69 and 138 volts on the primary
- 120 volts to the 240 tap
 - 12 V
 - Plus 60 and 104 volts on the primary

A Practical Moment

- I needed 24 VDC. I had a 48 Volt non regulated supply with a 120/240 volt input
- Solution: run the power supply on the 240 volt setting with 120 volts
 - The power supply is on all the time for control of an antenna
 - The supply is loaded only occasionally
- Benefits with 120 volts to the 240 setting:

• 120 volt connection	240 volt connection
• .25 amps	.11 amps
• 13 watts	4 watts
• 60 VDC	30VDC
- Saving 9 watts or about \$1 per month with continuous duty

Buck /Boost Configurations

- Each coil turn generates a voltage that can be added or subtracted to any other voltage on the transformer
 - This true for any combination of transformers. They do not have to have the same core or phase.
- 120 VAC to the 120 tap and 24 volts on the secondary there are 9 combinations!
 - $120 \pm 24 \text{ volts} = 96 \text{ or } 144 \text{ VAC}$
 - $208 \pm 24 \text{ volts} = 184 \text{ or } 232 \text{ VAC}$
 - $240 \pm 24 \text{ volts} = 216 \text{ or } 264 \text{ VAC}$
- 120 VAC to the 208 tap and 13.8 volts on the secondary:
 - $120 \pm 13.8, 69 \pm 13.8, 138 \pm 13.8$
- 120 VAC to the 240 tap and 12 volts on the secondary:
 - $120 \pm 12, 60 \pm 12, 104 \pm 12$

More!!!

- Connect the 120 volts to the 120 volt tap
- 208-120 gives 88 volts
 - In addition 88+/-24
- 240-208 gives 32 volts
 - In addition 32+/-24

Industrial Control Transformers

- Typically the primary is 240/480 volts
 - Dual windings that can be put in series or parallel
- Typically the secondary is 120/240 volts
 - Dual windings
- Lots of possibilities!
- Great 1:1 isolation transformers

Identifying Unknown Transformers

- Measure the winding resistances
 - The highest resistance is typically the highest voltage
 - It is generally safe to apply 120V to the highest voltages.
 - Most transformers are designed for 120, 240, or 480 volts
 - If in doubt:
 - Use a second transformer and apply 12 or 24 VAC
 - Use a 40 watt bulb in series with the power cord
- Weigh the transformer to estimate the power
 - A rule of thumb is each pound is good for 20 VA
 - A rule of the finger is if you can keep your finger on it for 15 seconds it is probably OK at about 140F
 - Use caution if there is a chance of a short to the core!

Testing Our Transformer

- Resistances
 - Red to green = 1.2 ohms (24 volts)
 - White to black = 19.9 ohms (120 volts)
 - White to red = 52 ohms (208 volts)
 - White to orange = 64.5 ohms (240 volts)
- Weight
 - Weight = 1.6 pounds
 - 1.6×20 watts per pound = 32 watts (rated 40watts)

A Practical Moment

- I needed to measure current going into my new amplifier. A current shunt on the DC side gave too low of a voltage to go into the Arduino micro computer.
 - 0 to .060 volts from the shunt
- Solution: removed the secondary winding of a old transformer and replace it with a 1 turn secondary.
 - 120 volts on the primary produced .24 volts on the secondary
 - Turns on the primary equals $120 / .24$ or 500 turns
- Current Through the 1 turn makes flux that creates a voltage on the old primary winding
- 15 amps AC yielded 20 volts on the old primary.
 - Voltage drop on the single turn is $20 / 500$ or .04 volts
 - The 20 volts is rectified and filtered to monitor the drain current of the amplifier and fed into the processor

Current Transformers

- Measuring large amounts of power having a voltage drop is typically unacceptable
 - This drop is due to the inductance of the single turn winding
- Current transformers are normally run with the secondary shorted
 - By shorting the secondary the flux of the primary is cancelled by the secondary

Clip on Amp Meters

- A common form of a current transformer with a single turn primary
 - If you need more sensitivity add more turns
 - 10 turns gives a multiplier of 10
 - There are no fractional turns!
- Only one lead goes through the meter
 - If both leads go through the meter the flux is cancelled if there is no leakage.
 - If there is leakage you will read the difference ie a GFI detector

A Practical Moment

- Looking for radiation on a feed line or RFI getting into extraneous equipment?
- Make up a current transformer out of a clip on choke
 - A bunch of turns on a clip on choke is the secondary
 - A diode and capacitor is the RF detector
 - Most any meter will read the current
- Move it up and down the line to read if and where common mode currents exist

A Practical Moment

- A choke type balun is form of a current transformer
- If net current (equal but opposite) is zero there is no flux created and therefore no reactance.
- If the currents are not equal it acts like a transformer adding voltage to low lead and subtracting voltage from the other
- To check what the balun is doing it can be disabled by a single shorted turn of wire. That will cancel any flux due to the unbalance currents

Questions ?

- More than you ever wanted to know about transformers!
- Discussion